

# DIGITAL LOGIC

## Chapter 3: Gate-Level Minimization

2025 Fall

This PowerPoint is for internal use only at Southern University of Science and Technology.  
Please do not repost it on other platforms without permission from the instructor.

# Today's Agenda

- Recap
- Context
  - Gate level minimization using the Map Method
  - Product of sums simplification
  - Don't Care Conditions
- Reading: Textbook, Chapter 3.1-3.5

# Recap

- Boolean Algebra
  - DeMorgan's Law:  $(x+y)'=x'y'$ ,  $(xy)'=x'+y'$
  - Distributivity:  $x(y+z)=xy+xz$ ;  $x+yz=(x+y)(x+z)$
  - Complements:  $x+x'=1$ ,  $x \cdot x'=0$
  - etc
- Boolean Functions
  - Literals, Product term, Sum term
  - Unique: Truth table ( $2^n$  entries for  $n$  variables)
  - Not unique: Algebraic forms (simplifiable to reduce literals/terms for cheaper circuits).
- Canonical & Standard Forms
  - Canonical (unique)
    - Sum of Minterms (som:  $\sum m_i$ , all variables)
    - Product of Maxterms (pom:  $\prod M_i$ ,  $M_i=m_i'$ )
  - Standard (not unique)
    - Sum of Products (SOP)
    - Product of Sums (POS)
- Other Logic Operations
  - Multi-input extension: AND/OR/XOR are associative; NAND/NOR are not.

# Outline

- **Map Method Simplification**
- Product of sums simplification
- Don't Care Conditions

# Boolean function simplification

- A function's truth-table representation is unique, while its algebraic expression is not unique.
- Complexity of digital circuit (gate count)  $\propto$  complexity of algebraic expression (literal count)
  - $F = x'y'z + x'yz + xy'$  (3 Product/AND term, 8 literals)
  - $F = x'z + xy'$  (2 AND terms, 4 literals)
- The simplest algebraic expression is one that has minimum number of terms with the smallest possible number of literals in each term
- Methods for gate-level minimization:
  - **Algebraic method**(逻辑代数): Boolean algebra (Last lecture)
  - **Karnaugh map**(卡诺图): the map method (This lecture)

# Karnaugh Map (K-map)

- An array of squares each representing one minterm to be minimized
- Each K-map defines a unique Boolean function
  - A Boolean function can be represented by a truth table, a Boolean expression, or a map
- K-map is a visual diagram of all possible ways a function may be expressed
- Used for manual minimization of Boolean functions



# Merging Minterms

- In function  $F$ ,  $m_1$  and  $m_3$  in the truth table differ only in one position
  - $001 \rightarrow x'y'z$
  - $011 \rightarrow x'yz$
  - $0?1$ , with ? matching either 0 or 1, meaning the value of input  $y$  does not affect the function's output.
- The minterms in a function can be merged to form a simpler product term
  - $F = x'y'z + x'yz = x'z(y' + y) = x'z$


x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0
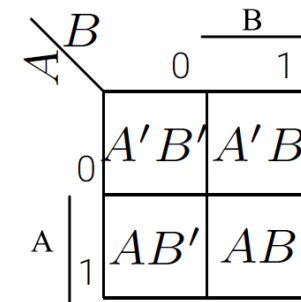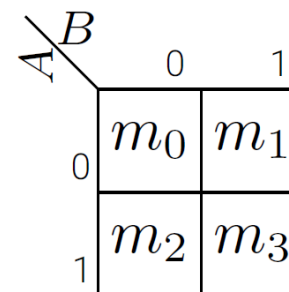
# Two-Variable Map

- A two-variable map
  - is A truth table in square diagram
  - 4 minterms:  $A'B'$ ,  $A'B$ ,  $AB'$ ,  $AB$
  - row 0 stands for  $A'$ ; row 1 stands for  $A$
  - column 0 stands for  $B'$ ; column 1 stands for  $B$



	A	B	F
$m_0$	0	0	0
$m_1$	0	1	1
$m_2$	1	0	1
$m_3$	1	1	1

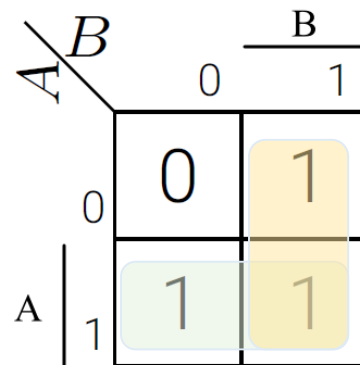

It's ok for groups to overlap, if that makes them larger

$$m_1 + m_2 + m_3 = A'B + AB' + AB = A + B$$



# Three-variable Map



- Minterms are arranged in the Gray-code sequence
- Any 2 (horizontally or vertically) adjacent squares differ by exactly 1 variable, which is complemented in one square and uncomplemented in the other.
- Any 2 minterms in adjacent squares that are ORed together will cause a removal of the different variable (adjacent applies not only the middle squares but also the boundary squares)

		B			
		00	01	11	10
A	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$

C

# Three-variable Map

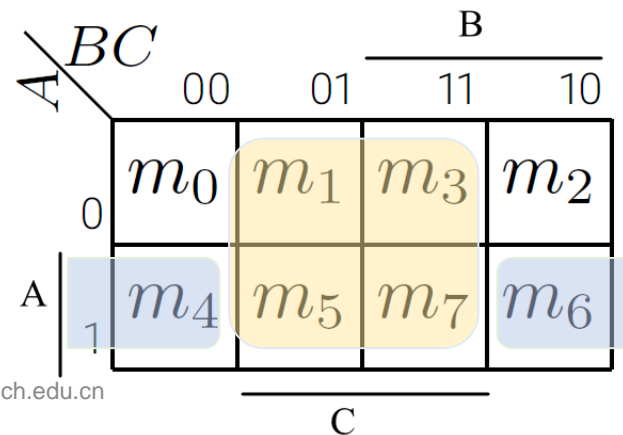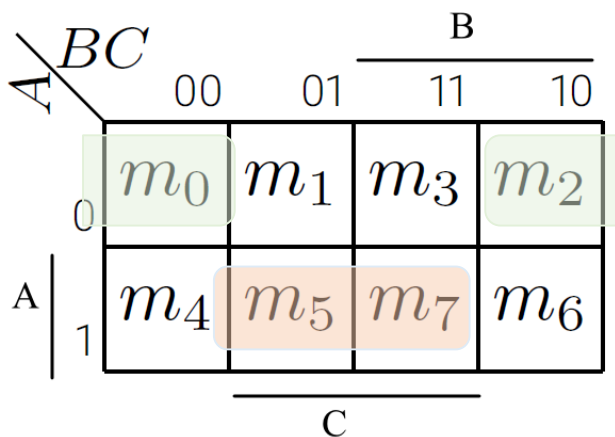- Example (adjacent squares)
- $m_5 + m_7 = AB'C + ABC = AC(B + B') = AC$
- $m_0 + m_2 = A'B'C' + A'BC' = A'C'(B + B') = A'C'$
- $m_4 + m_6 = AB'C' + ABC' = AC'(B' + B) = AC'$
- $m_1 + m_3 + m_5 + m_7$   
 $= A'B'C + A'BC + AB'C + ABC = A'C(B + B') + AC(B + B')$   
 $= A'C + AC = C$



# Example

- Simplify the following Boolean functions.

$$F = A'BC + A'BC' + AB'C' + AB'C$$

$$= A'B + AB'$$

		B			
		00	01	11	10
A	0	0	0	1	1
	1	1	1	0	0

C

Green circle:  $A'BC + A'BC' = A'B$   
 Red circle:  $AB'C' + AB'C = AB'$

$$F = A'BC + AB'C' + ABC' + ABC$$

$$= BC + AC'$$

		B			
		00	01	11	10
A	0	0	0	1	0
	1	1	0	1	1

C

Green circle:  $A'BC + ABC = BC$   
 Red circle:  $AB'C' + ABC' = AC'$

# Example

- Simplify the following Boolean functions.

$$F = \sum(1, 2, 3, 5, 7) = C + A'B$$

		B			
		BC			
A	0	0	1	1	1
	1	0	1	1	0

Groups: A horizontal group of four 1s (minterms 1, 2, 3, 5) is highlighted in red and labeled C. A vertical group of two 1s (minterms 1, 5) is highlighted in green and labeled A'B.

$$F = \sum(0, 2, 4, 5, 6) = C' + AB'$$

		B			
		BC			
A	0	1	0	0	1
	1	1	1	0	1

Groups: A horizontal group of four 1s (minterms 0, 2, 4, 6) is highlighted in red and labeled C'. A vertical group of two 1s (minterms 0, 2) is highlighted in green and labeled AB'.

It's ok for groups to overlap, if that makes them larger

# Exercise

- Simplify the following Boolean function.
  - $F = A'C + A'B + AB'C + BC$   
= ?


# Exercise

- Simplify the following Boolean function.
  - $F = A'C + A'B + AB'C + BC = ?$
- Solution:
  - Express it in sum of minterms.
  - Find the minimal sum of products expression.
  - $F = A'C + A'B + AB'C + BC$ 

$$= A'C(B+B') + A'B(C+C') + AB'C + (A+A')BC$$

$$= A'BC + A'B'C + A'BC + A'BC' + AB'C + ABC + A'BC$$

$$= \Sigma(1, 2, 3, 5, 7) = C + A'B$$

		B			
		00	01	11	10
A	0	0	1	1	1
	1	0	1	1	0

C

# Four-Variable Map

- The map
  - 16 minterms
  - Combinations of 2, 4, 8, and 16 adjacent squares

		C			
		00	01	11	10
A	00	$m_0$	$m_1$	$m_3$	$m_2$
	01	$m_4$	$m_5$	$m_7$	$m_6$
	11	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
	10	$m_8$	$m_9$	$m_{11}$	$m_{10}$
		D			

# Implicants

- Implicant: any product term that implies the function

- A product term that makes a function to be true

	minterm	implicant
$m_1$	✓	✓
$m_2$	✓	X
$x'z$	X	✓

1-minterm

0-minterm

1 product term

- Prime implicant (PI) (质蕴含)

- A 1-product term obtained by combining the maximum possible number of adjacent squares in the map.

- Essential prime implicant (EPI) (基本质蕴含)

- If a minterm in a square is covered by only one prime implicant

x	y	z	F	
0	0	0	0	$m_0$
0	0	1	1	$m_1$
0	1	0	0	$m_2$
0	1	1	1	$m_3$
1	0	0	1	$m_4$
1	0	1	1	$m_5$
1	1	0	0	$m_6$
1	1	1	0	$m_7$





# Tips for simplification

- Simplification Steps:
  - Determine all essential prime implicants.
  - Find other prime implicants that cover remaining minterms.
  - Logical sum all prime implicants.
- Tips:
  1. Adjacent Coverage(相邻覆盖): Loop adjacent 1s, making each loop as large as possible.
  2. Minimal Loops(最少圈数): Use the fewest loops to cover all 1s for simplification.
  3. Avoid Redundancy(避免冗余): Ensure each loop covers at least one unique 1 not covered by other loops.
  4. Boundary Connectivity(边界连通): Treat the map as continuous—left/right and top/bottom edges are adjacent.
  5. Power-of-Two Priority(幂次优先): Prioritize looping groups of  $2^n$  1s (e.g., 8, 4, 2, 1) for maximum simplification.
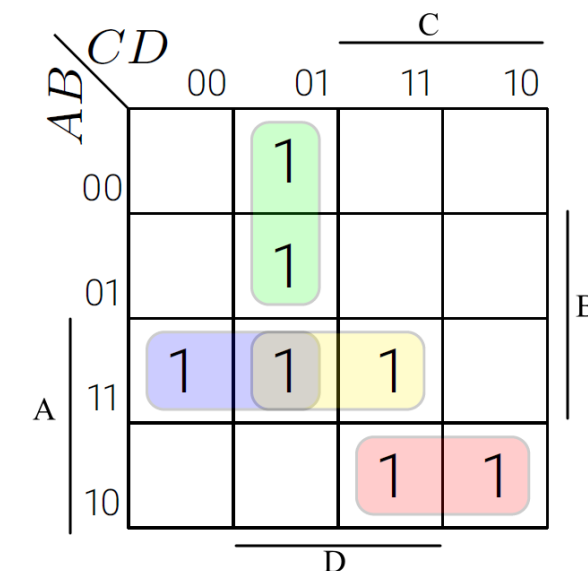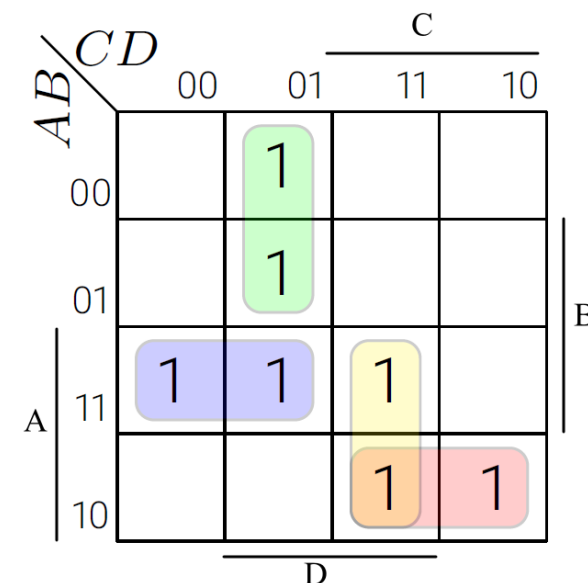
# Example

- Simplify the following Boolean functions
- $F = m_1 + m_5 + m_{10} + m_{11} + m_{12} + m_{13} + m_{15}$ 
  - start with EPIs
  - Green circle:  $A'B'C'D + A'BC'D = A'C'D$
  - Purple circle:  $ABC'D' + ABC'D = ABC'$
  - Red circle: ...
  - ...
- $F = A'C'D + ABC' + ACD + AB'C$
- This reduced expression is not a unique one
  - If pairs are formed in different ways, the simplified expression will be different.
  - $F = A'C'D + ABC' + ABD + AB'C$




# Example

- Simplify the following Boolean functions.

$$F = \sum(7, 9, 10, 11, 12, 13, 14, 15)$$

$$= AB + AC + AD + BCD$$

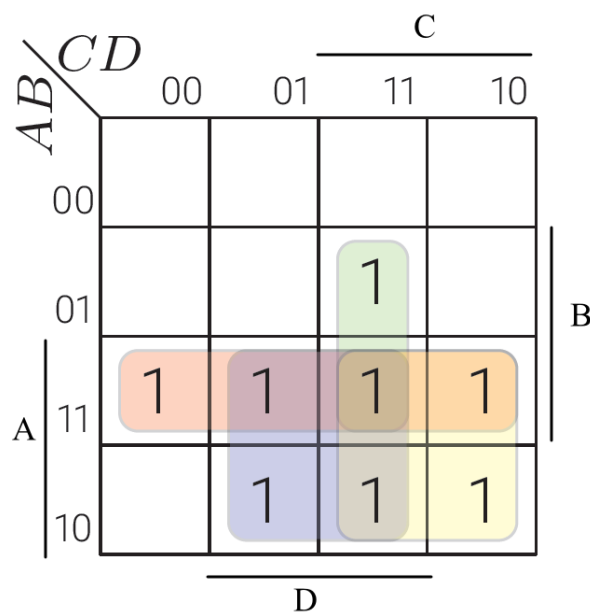

$$F(A,B,C,D) = ABCD + AB'C'D' + AB'C + AB$$


$$= ABCD + AB'C'D' + AB'C(D + D')$$

$$+ AB(C + C')(D + D')$$

$$= \dots$$

$$= \sum(8, 10, 11, 12, 13, 14, 15)$$

$$= AB + AC + AD'$$

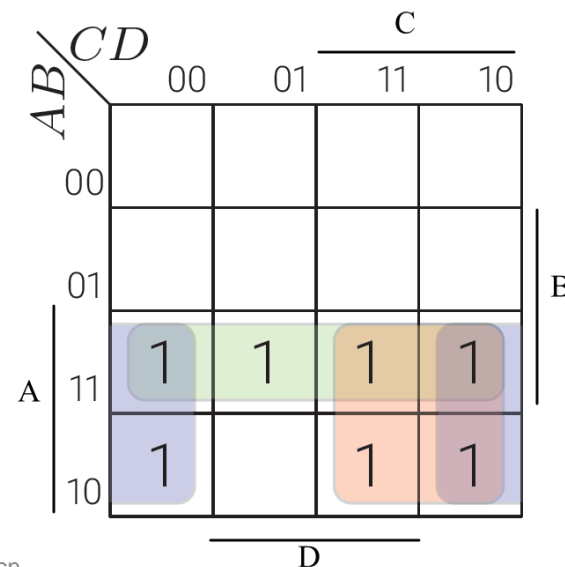

# Exercise

- Simplify the following Boolean functions.


$$\begin{aligned} F(A,B,C,D) \\ &= \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14) \\ &= ? \end{aligned}$$


$$\begin{aligned} F(A,B,C,D) \\ &= A'B'C' + B'CD' + A'BCD' + AB'C' \\ &= ? \end{aligned}$$

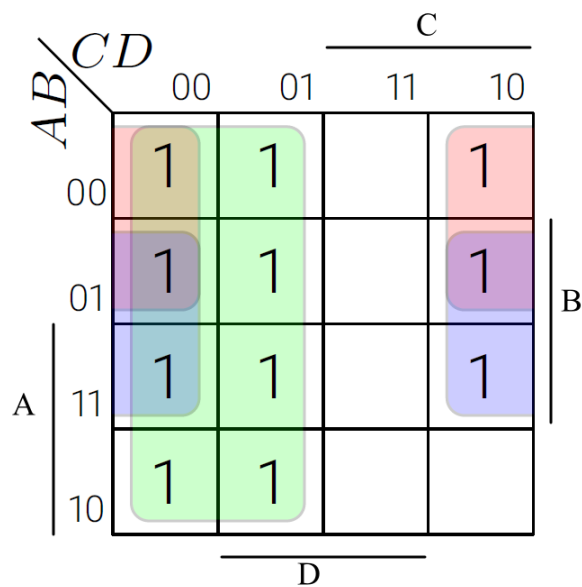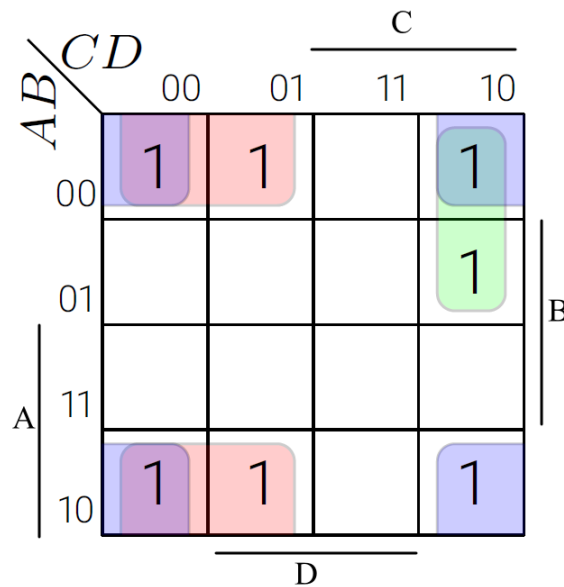

# Exercise

- Simplify the following Boolean functions.

$$\begin{aligned} F(A,B,C,D) &= \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14) \\ &= C' + A'D' + BD' \end{aligned}$$



$$\begin{aligned} F &= A'B'C' + B'CD' + A'BCD' + AB'C' \\ &= A'B'C'(D + D') + B'CD'(A + A') + \\ &\quad A'BCD' + AB'C'(D + D') \\ &= A'B'C'D + A'B'C'D' + AB'CD' + A'B'CD' + \\ &\quad A'BCD' + AB'C'D + AB'C'D' \\ &= \sum(0, 1, 2, 6, 8, 9, 10) \\ &= B'C' + B'D' + A'CD' \end{aligned}$$



# K-map Summary

- Any  $2^k$  adjacent squares,  $k=0,1,...,n$ , in an  $n$ -variable map represent an area that gives a product term of  $n-k$  literals

K	# of adjacent squares	# of literals left in a term in an n-variable map		
		n=2	n=3	n=4
0	1	2	3	4
1	2	1	2	3
2	4	0	1	2
3	8		0	1
4	16			0

- Five-Variable Map
  - Map for more than four variables becomes complicated
  - Five-variable map: two four-variable map (one on the top of the other), contains  $2^5$  or 32 cells.

# Outline

- Map Method Simplification
- **Product of sums simplification**
- Don't Care Conditions

# Product of Sums Simplification

- Previous Examples are Sum of Product Simplification
  - E.g.  $F = AB + A'D + AB'C$  (Product of sum form)
- How to find Product of Sum simplification
  - E.g.  $F = (A+B)(B+C')$  (Sum of Product form)
- POS simplification Steps
  - Simplified  $F'$  in the form of sum of products
    - Group adjacent 0-minterms squares together
  - Apply DeMorgan's theorem  $F = (F')'$
  - $F'$ : sum of products  $\rightarrow$   $F$ : product of sums



# Example

- Simplify the Boolean function into product of sums form:

- $F(A,B,C,D) = \sum(2, 3, 7, 10, 11, 15)$

- Solution

- Step1: group the 0-minterms to find **F complement**

$$\begin{aligned} F' &= \sum(0, 1, 4, 5, 6, 8, 9, 12, 13, 14) \\ &= C' + BD' \quad (\text{Group 0 minterms}) \end{aligned}$$

- Step2: find the complement again to get original F

$$\begin{aligned} F &= (F')' = (C' + BD')' \\ &= C(B' + D) \quad (\text{DeMorgan's}) \end{aligned}$$

		C			
		D			
A	B	CD			
		00	01	11	10
A	00	0	0	1	1
	01	0	0	1	0
	11	0	0	1	0
	10	0	0	1	1

# Exercise

- simplify  $F(A, B, C, D) = \sum(0, 1, 2, 5, 8, 9, 10)$  into
  - sum-of-products form
    - $F = ?$
  - product-of-sums form
    - $F = ?$



# Exercise

- simplify  $F(A, B, C, D) = \sum(0, 1, 2, 5, 8, 9, 10)$  into
  - sum-of-products form
    - $F = B'D' + B'C' + A'C'D$  (Group 1-minterms)
  - product-of-sums form
    - $F' = AB + CD + BD'$  (Group 0-minterms)
    - $F = (A'+B')(C'+D')(B'+D)$  (DeMorgan's)

		CD		C	
		00	01	11	10
A	AB	00	01	11	10
	00	1	1	0	1
	01	0	1	0	0
	11	0	0	0	0
	10	1	1	0	1
		D			

B

		CD		C	
		00	01	11	10
A	AB	00	01	11	10
	00	1	1	0	1
	01	0	1	0	0
	11	0	0	0	0
	10	1	1	0	1
		D			

B

# Outline

- Map Method Simplification
- Product of sums simplification
- **Don't Care Conditions**

# Don't care conditions

- Incompletely specified functions
  - Functions that have unspecified outputs for some input combinations
  - E.g. output are unspecified for 1010 to 1111 in 4-bit BCD code
- Don't-care conditions
  - Unspecified minterms of a function, don't-cares, Xs
  - Can be used on a map to provide further simplifications of the Boolean expression
  - Each X can be assigned an arbitrary value, 0 or 1, to help simplification procedure

# Example

- Simplify  $F(A, B, C, D) = \sum(1, 3, 7, 11, 15)$  with don't-care conditions  $d(A, B, C, D) = \sum(0, 2, 5)$ .
  - $F = A'B' + CD$
  - or  $F = A'D + CD$
  - Just make sure all 1 minterms are circled, thus both simplifications are acceptable

		C			
		00	01	11	10
A	00	X	1	1	X
	01		X	1	
	11			1	
	10			1	
		D			


Diagram illustrating a Karnaugh map for the function  $F(A, B, C, D)$ . The map shows minterms 1, 3, 7, 11, and 15 as 1s, and don't-care conditions 0, 2, and 5 as Xs. The map is organized with A as the vertical axis and B as the horizontal axis. The columns are labeled CD (00, 01, 11, 10) and the rows are labeled AB (00, 01, 11, 10). The 1s are circled in green (forming  $A'B'$ ) and red (forming  $CD$ ).

		C			
		00	01	11	10
A	00	X	1	1	X
	01		X	1	
	11			1	
	10			1	
		D			

Diagram illustrating a Karnaugh map for the function  $F(A, B, C, D)$ . The map shows minterms 1, 3, 7, 11, and 15 as 1s, and don't-care conditions 0, 2, and 5 as Xs. The map is organized with A as the vertical axis and B as the horizontal axis. The columns are labeled CD (00, 01, 11, 10) and the rows are labeled AB (00, 01, 11, 10). The 1s are circled in green (forming  $A'D$ ) and red (forming  $CD$ ).
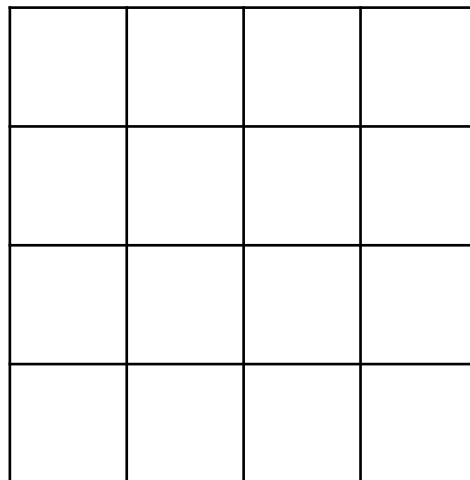
# Exercise

- Using the Karnaugh map method obtain the minimal sum of the products expression for the function  $F(A,B,C,D) = \Sigma(0, 2, 3, 6, 7) + d(8, 10, 11, 15)$



# Exercise

- Using the Karnaugh map method obtain the minimal sum of the products expression for the function  $F(A,B,C,D) = \Sigma(0, 2, 3, 6, 7) + d(8, 10, 11, 15)$
- $F = A'C + B'D'$

		CD					
		00	01	11	10	C	
A	00	1	0	1	1	B	
	01	0	0	1	1		
	11	0	0	X	0		
	10	X	0	X	X	D	