

Digital Logic - Assignment I

1. Simplify the following four-variable Boolean functions to simplest POS form using K-map method:
 $F(A,B,C,D) = \Pi(0, 2, 6, 11, 13, 14, 15) + d(1, 3, 9, 10, 12)$.

AB\CD	00	01	11	10
00	0	X	X	0
01	1	1	1	0
11	X	0	0	0
10	1	X	0	X

Simplification method:

☐ Group the 1-cells to get the simplest SOP for F

☒ Group the 0-cells to get the SOP for F', then use De Morgan's law to get the POS for F.

Enter Boolean Expression:

(A+B)(C'+D)(A'+D')

Submit

Brush Tools

Color Selection

Value Brushes

0

1

X

Actions

You are simplifying based on cells with value 0 (F').

Current: Color Brush

Use a different color for each prime implicant (circled group). The circles wrap around the boundary still count as a single group

Tip: Hold the left mouse button and drag on the grid to select an area

2. Obtain the simplified Boolean expressions for output F1 and F2 in terms of the input variables in the following circuit.

F1

1 = $((AB)'((A+B)')) \oplus (C)'$

×

2 = $(A'+B')(A+B) \oplus C$

×

3 = $(A'B+AB') \oplus C$

×

4 = $C(A'B+AB')' + C'(A'B+AB')$

×

5 = $C(A+B')(A'+B) + A'BC' + AB'C'$

×

6 = $ABC + A'B'C + A'BC' + AB'C'$

×

7 = $C(AB+A'B') + C'(A'B+AB')$

×

Add simplification step (or press Enter)

Allowed Variables:

A

B

C

Please add ' after subscript, e.g., Q_{t+1}

Simplify the following expression:

F2

- 1

=

((AB)'C'+(A+B))'

×
- 2

=

(AB+C)(A+B)

×
- 3

=

AB+AC+BC

×
- 4

=

A(B+C)+BC

×

Add simplification step (or press Enter)

Please add ' after subscript, e.g., Qt+1'

Allowed Variables:

A B C

A	B	C	T1	T2	T3	T4	F1	F2
0	0	0	1	1	1	0	0	0
0	0	1	1	1	0	0	1	0
0	1	0	1	0	1	1	1	0
0	1	1	1	0	0	1	0	1
1	0	0	1	0	1	1	1	0
1	0	1	1	0	0	1	0	1
1	1	0	0	0	0	0	0	1
1	1	1	0	0	0	0	1	1

3. Design a combinational circuit with three inputs, x, y, and z, and three outputs, A, B, and C. When the binary input is 0, 1, or 2, the binary output is two greater than the input. When the binary input is 3, 4, 5, 6, or 7, the binary output is one less than the input. You need to provide:

x	y	z	A	B	C
0	0	0	0	1	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0

x\yz	00	01	11	10
0	0	0	0	1
1	0	1	1	1

Simplification method:

- ☒ Group the 1-cells to get the simplest SOP for F
- ☐ Group the 0-cells to get the SOP for F', then use De Morgan's law to get the POS for F.


Enter Boolean Expression:

xz+yz'

Submit

Brush Tools

Color Selection

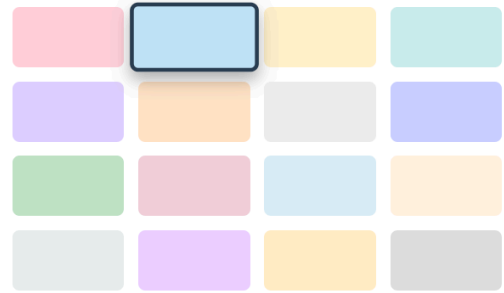

Value Brushes



Actions

You are simplifying based on cells with value **1** (F).

Current:  Color Brush

x\yz	00	01	11	10
0	1	1	1	0
1	1	0	1	0

Simplification method:

- ☒ Group the 1-cells to get the simplest SOP for F
- ☐ Group the 0-cells to get the SOP for F', then use De Morgan's law to get the POS for F.

Enter Boolean Expression:

y'z'+x'y'+yz

Submit

Brush Tools

Color Selection



Value Brushes



Actions

You are simplifying based on cells with value **1** (F).

Current:  Color Brush

x\yz	00	01	11	10
0	0	1	0	0
1	1	0	0	1

Simplification method:

- ☒ Group the 1-cells to get the simplest SOP for F
- ☐ Group the 0-cells to get the SOP for F', then use De Morgan's law to get the POS for F.

Enter Boolean Expression:

x'y'z+xz'

Submit

Brush Tools

Color Selection

Value Brushes

0

1


X


Actions

You are simplifying based on cells with value **1** (F).


Current: Color Brush

线很乱可能难以辨认，建议直接对着 expression 自己画一下，很简单。

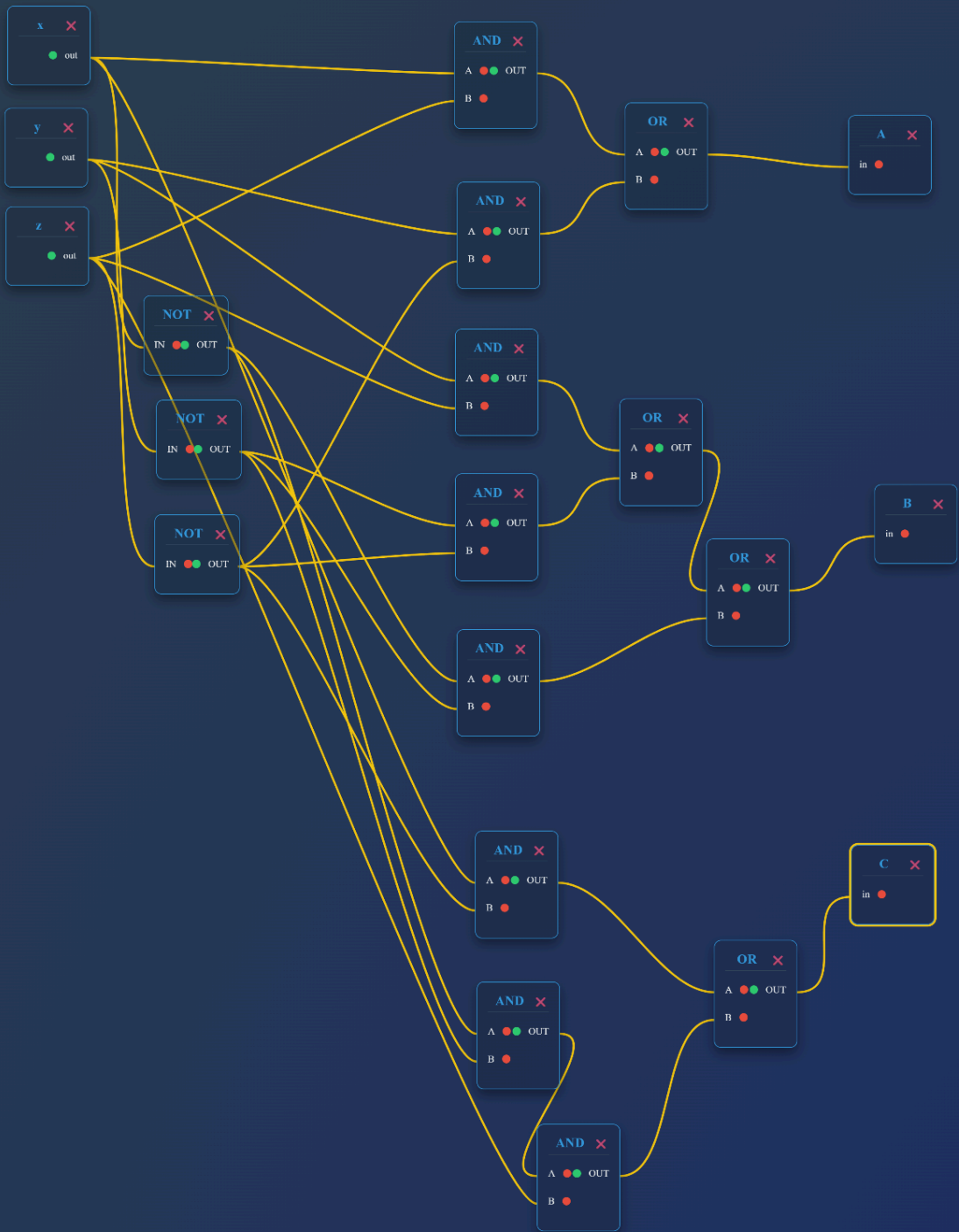

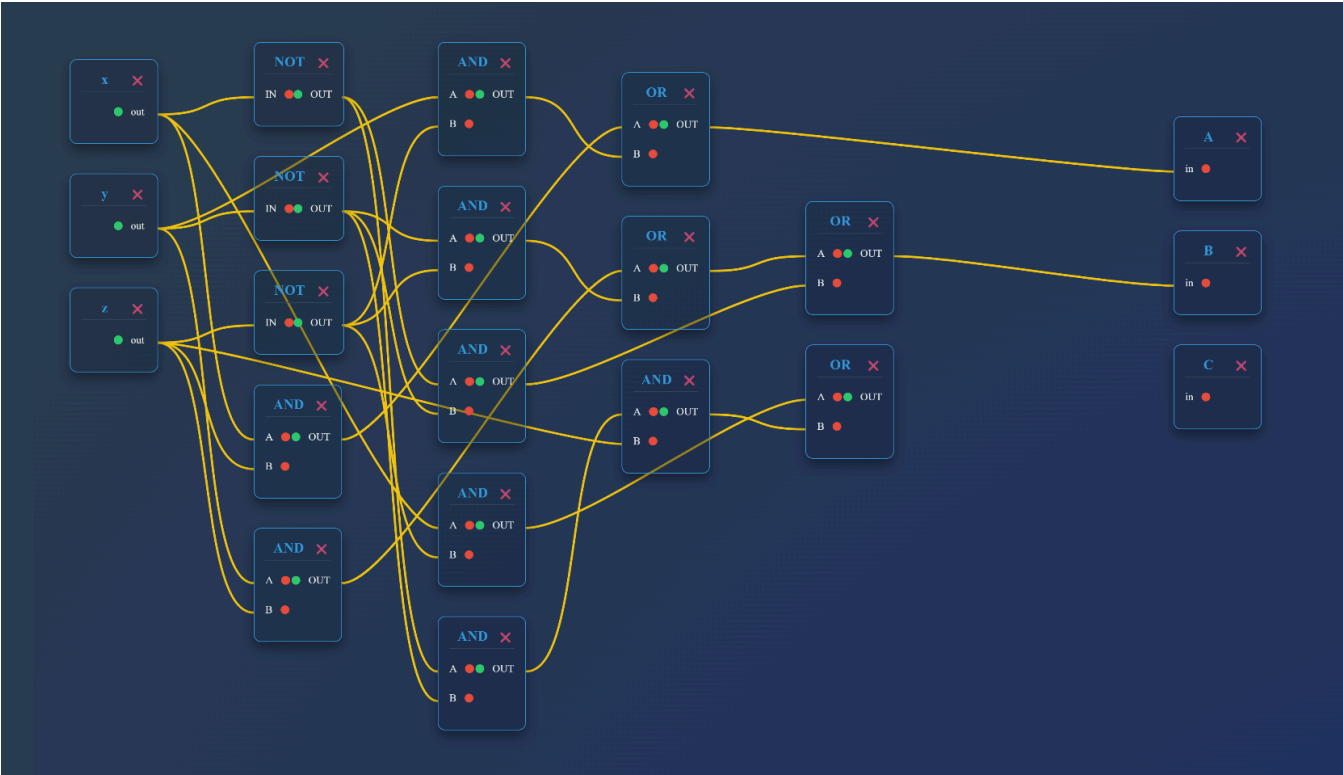

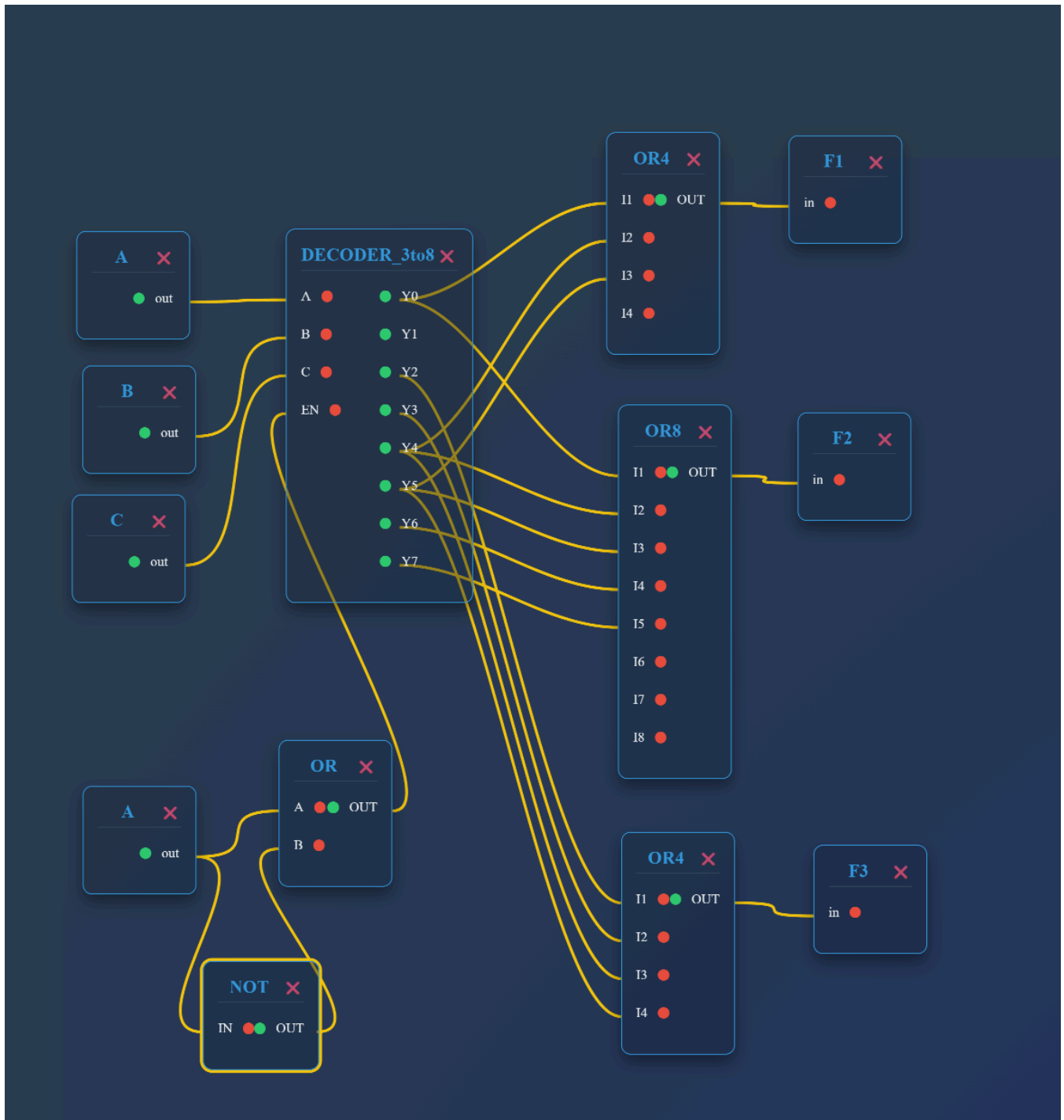4. A combinational circuit is defined by the equations $F1=AB+A'B'C'$ $F2=A+B+C'$ $F3=A'B+AB'$ Design a circuit which implements these three equations using a decoder and OR gates external to the decoder, and draw the logic diagram.



5. An 8:1 multiplexer has inputs A, B, and C connected to the selection inputs S2, S1, and S0, respectively. The data inputs I0 through I7 are as follows: $I_1=I_2=0$; $I_3=I_5=I_7=1$; $I_0=I_4=D$; and $I_6=D'$. Determine the Boolean function $F(A, B, C, D)$ that the multiplexer implements. You need to:

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1

1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

AB\CD	00	01	11	10
00	0	1	0	0
01	0	0	1	1
11	1	0	1	1
10	0	1	1	1

Simplification method:

- ☒ Group the 1-cells to get the simplest SOP for F
- ☐ Group the 0-cells to get the SOP for F', then use De Morgan's law to get the POS for F.


Enter Boolean Expression:

AC+BC+B'C'D+ABD'

Submit

Brush Tools

Color Selection

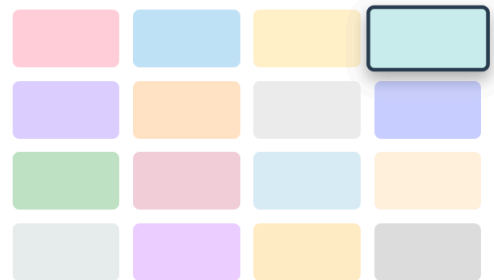


Value Brushes



Actions

You are simplifying based on cells with value **1** (F).

Current: Color Brush

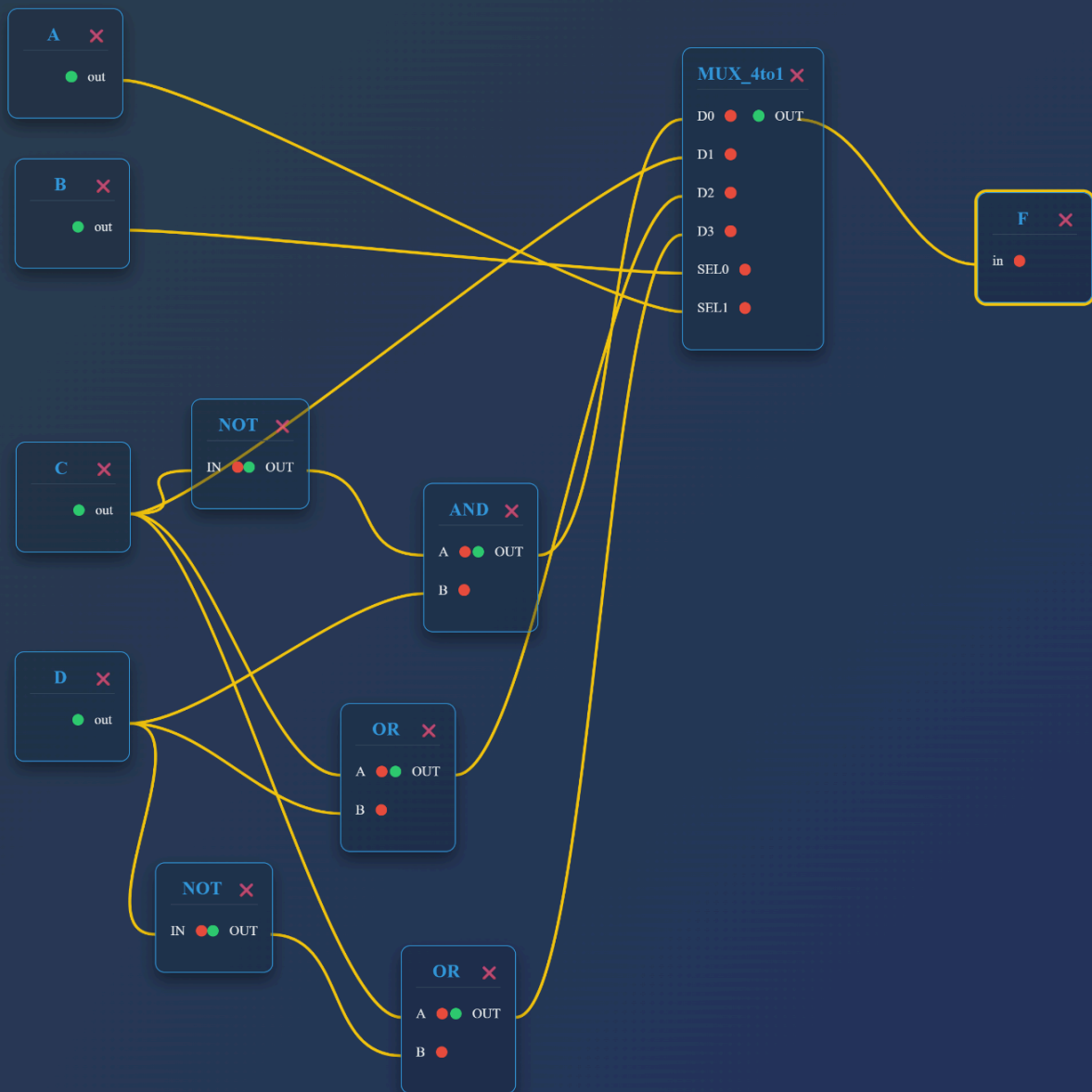

6. Construct a 16x1 multiplexer with two 8x1 and one 4x1 multiplexers.

