

# DIGITAL LOGIC

## Chapter 4 part2: Standard Components

2025 Fall

This PowerPoint is for internal use only at Southern University of Science and Technology.  
Please do not repost it on other platforms without permission from the instructor.

# Today's Agenda

- Recap
- Context
  - Decoder
  - Multiplexer
  - Encoder
- Reading: Textbook, Chapter 4.9-4.11

# Recap

- Combinational Circuits
  - Memoryless: Outputs depend only on current inputs
  - Common Examples: Adders, comparators, decoders, multiplexers
- Analysis Methods
  - Truth Table Approach
    - List all input combinations
    - Derive outputs step by step
  - Algebraic Approach
    - Label gate outputs
    - Write Boolean functions
    - Simplify expressions
- Design Procedure
  - Specification - Define inputs/outputs
  - Formulation - Derive truth table
  - Optimization - Simplify using K-maps
  - Implementation - Draw logic diagram

# Outline

- **Decoder**
- Multiplexer
- Encoder


# One-hot Representation

- Represent a set of N elements with N bits
- Exactly one bit is set

| Binary | One-hot  |
|--------|----------|
| 000    | 00000001 |
| 001    | 00000010 |
| 010    | 00000100 |
| 011    | 00001000 |
| 100    | 00010000 |
| 101    | 00100000 |
| 110    | 01000000 |
| 111    | 10000000 |
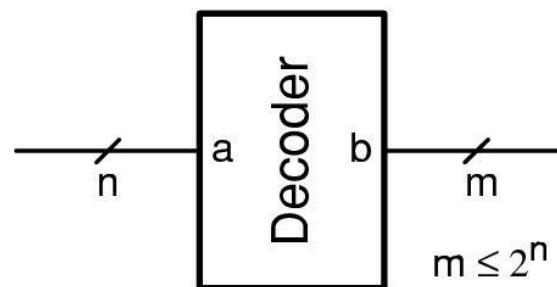
# Decoder

- A decoder is a combinational circuit that converts binary information from  $n$  input lines to  $m$  (maximum of  $2^n$ ) unique output lines
  - $n$ -to- $m$ -line decoder
- A binary one-hot decoder converts a symbol from binary code to a one-hot code
  - Output variables are mutually exclusive because only one output can be equal to 1 at any time (the 1-minterm)
- Example
  - binary input  $a$  to one-hot output  $b$
  - $b[i] = 1$  if  $a = i$  or  $b = 1 \ll a$
  - $a$  stands for position of 1 in  $b$



# 1-to-2-Line Decoder

- Step1: Specification
- Step2: Formulation

| x | D <sub>1</sub> | D <sub>0</sub> |
|---|----------------|----------------|
| 0 | 0              | 1              |
| 1 | 1              | 0              |


- Step3: Optimization

$$D_0 = x'$$

$$D_1 = x$$

↙ minterms  
↘

- Step4: Logic Diagram

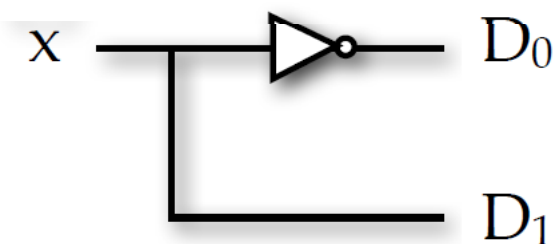


# 2-to-4-Line Decoder

Step 1,2


| $a_1$ | $a_0$ | $b_3$ | $b_2$ | $b_1$ | $b_0$ |
|-------|-------|-------|-------|-------|-------|
| 0     | 0     | 0     | 0     | 0     | 1     |
| 0     | 1     | 0     | 0     | 1     | 0     |
| 1     | 0     | 0     | 1     | 0     | 0     |
| 1     | 1     | 1     | 0     | 0     | 0     |

Step 3

$$\begin{aligned} b_3 &= a_1 a_0 \\ b_2 &= a_1 a_0' \\ b_1 &= a_1' a_0 \\ b_0 &= a_1' a_0' \end{aligned}$$

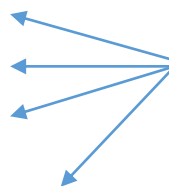
 minterms

Step 4

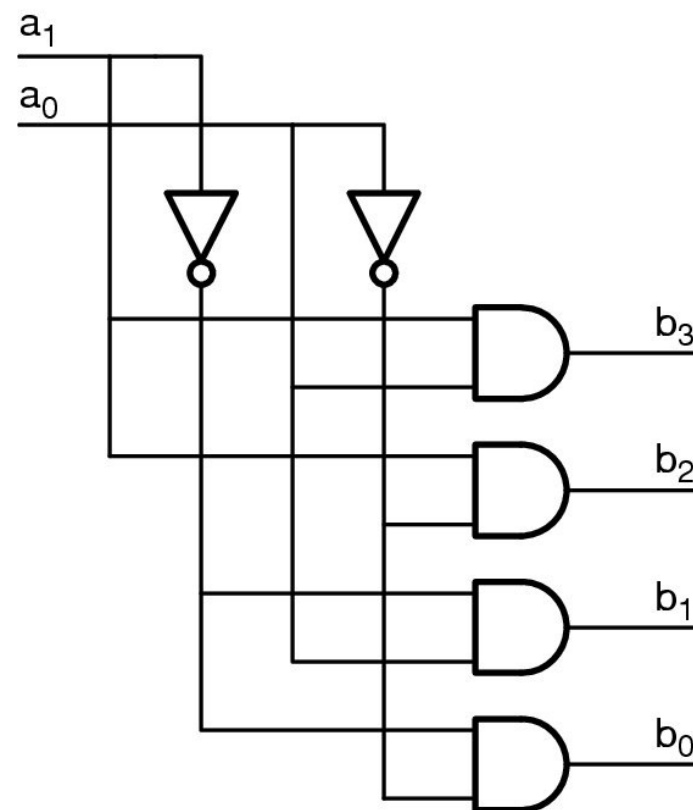




# 3-to-8-Line Decoder

- Each output of the decoder represents one of the eight minterms of the Boolean function

Step 1,2



| Inputs |     |     | Outputs |       |       |       |       |       |       |       |
|--------|-----|-----|---------|-------|-------|-------|-------|-------|-------|-------|
| $x$    | $y$ | $z$ | $D_0$   | $D_1$ | $D_2$ | $D_3$ | $D_4$ | $D_5$ | $D_6$ | $D_7$ |
| 0      | 0   | 0   | 1       | 0     | 0     | 0     | 0     | 0     | 0     | 0     |
| 0      | 0   | 1   | 0       | 1     | 0     | 0     | 0     | 0     | 0     | 0     |
| 0      | 1   | 0   | 0       | 0     | 1     | 0     | 0     | 0     | 0     | 0     |
| 0      | 1   | 1   | 0       | 0     | 0     | 1     | 0     | 0     | 0     | 0     |
| 1      | 0   | 0   | 0       | 0     | 0     | 0     | 1     | 0     | 0     | 0     |
| 1      | 0   | 1   | 0       | 0     | 0     | 0     | 0     | 1     | 0     | 0     |
| 1      | 1   | 0   | 0       | 0     | 0     | 0     | 0     | 0     | 1     | 0     |
| 1      | 1   | 1   | 0       | 0     | 0     | 0     | 0     | 0     | 0     | 1     |

Step 4

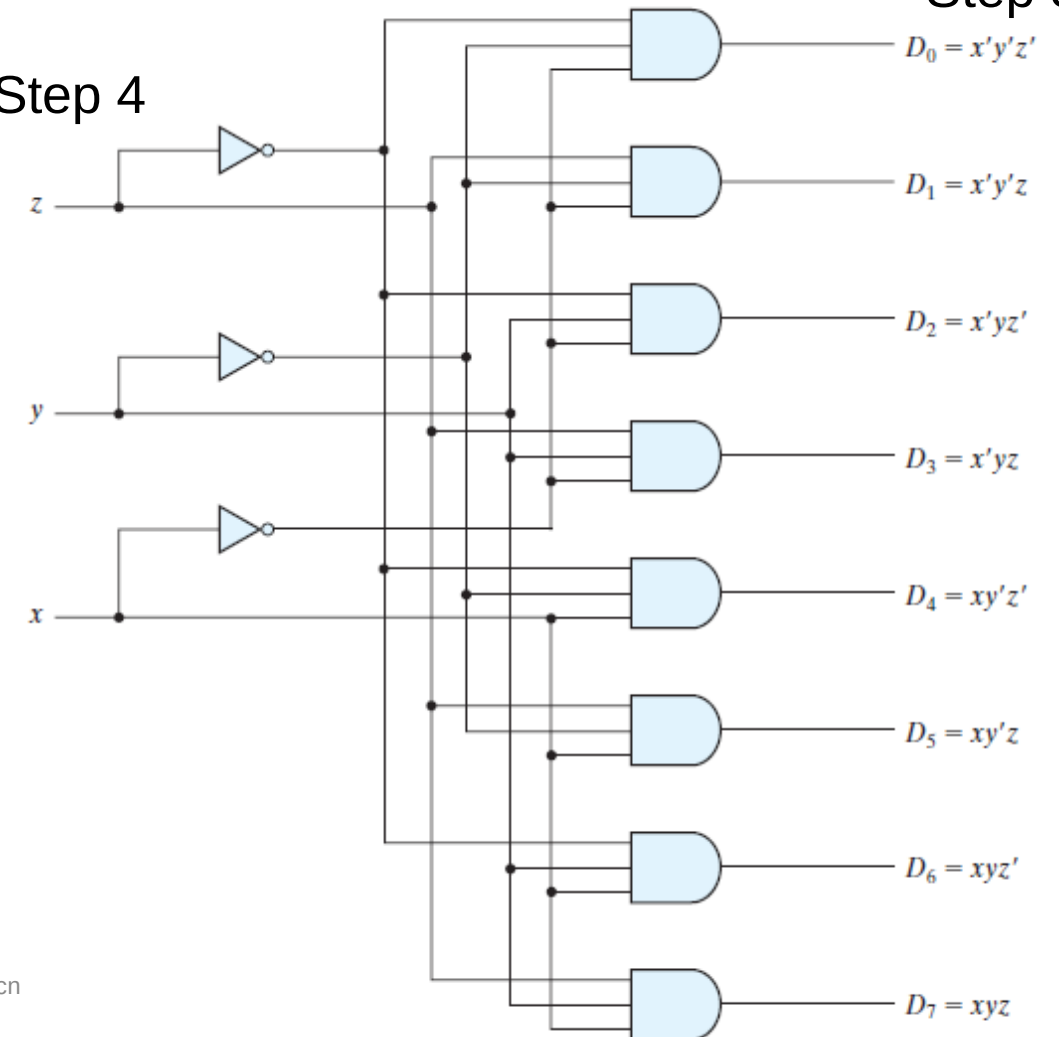
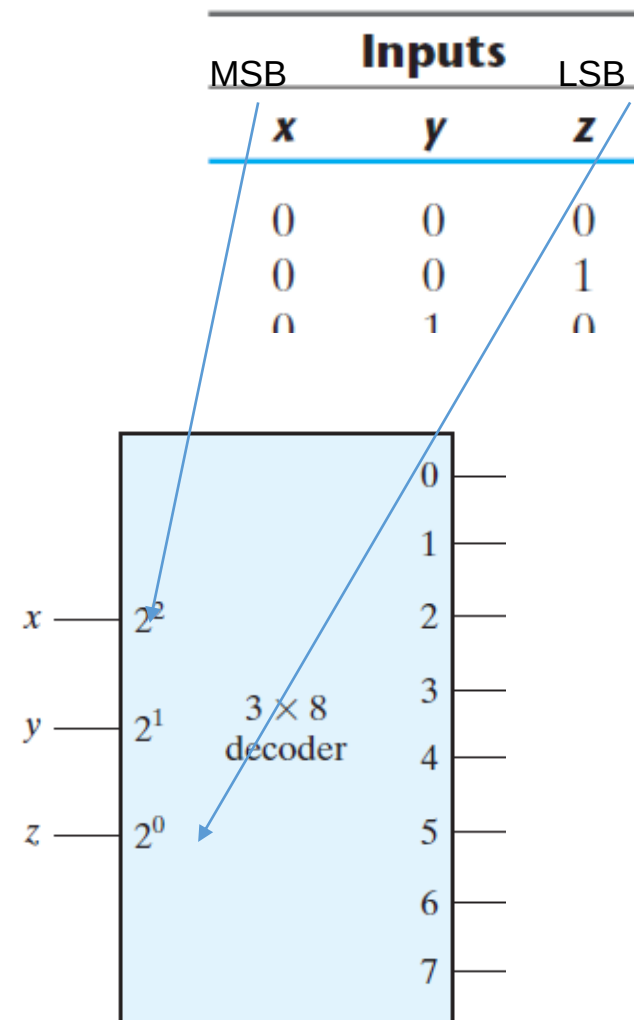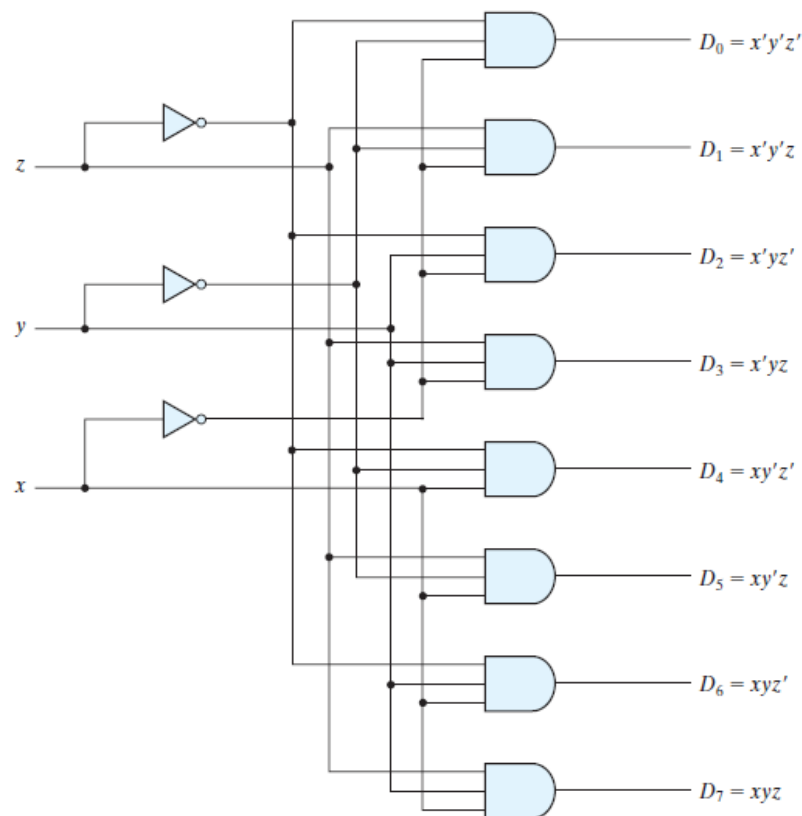
# Graphic Symbol of Decoder

- We can use graphic symbol/block diagram
  - You must clearly denoting the input and output within decoder's box



# Main Usages of Decoders

- Minterm generator:
  - Generate the  $2^n$  (or fewer) minterms of  $n$  input variables. For example: a 3-8 line decoder
- Data demultiplexing:
  - A decoder with enable input can function as a demultiplexer – a circuit that receives information from a single line and directs it to one of  $2^n$  possible output lines.
- Display decoding:
  - Decoders are used in display systems to select a specific output line based on the input code and drive the corresponding segment of the display.
- Address decoding:
  - Identify a memory cell, disk sector, or other memory or storage device, to ensure one device can communicate with the processor at one time.

# Decoder for logic implementation


## Example1

- Decoder can be used to implement the logic function by connecting the appropriate minterms to an OR gate.
  - Any combinational circuit with  $n$  inputs and  $m$  outputs can be implemented with an  $n$ -to- $2^n$  decoder in conjunction with  $m$  external OR gates

| x | y | z | C | S |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

$$S(x, y, z) = \sum(1, 2, 4, 7)$$

$$C(x, y, z) = \sum(3, 5, 6, 7)$$

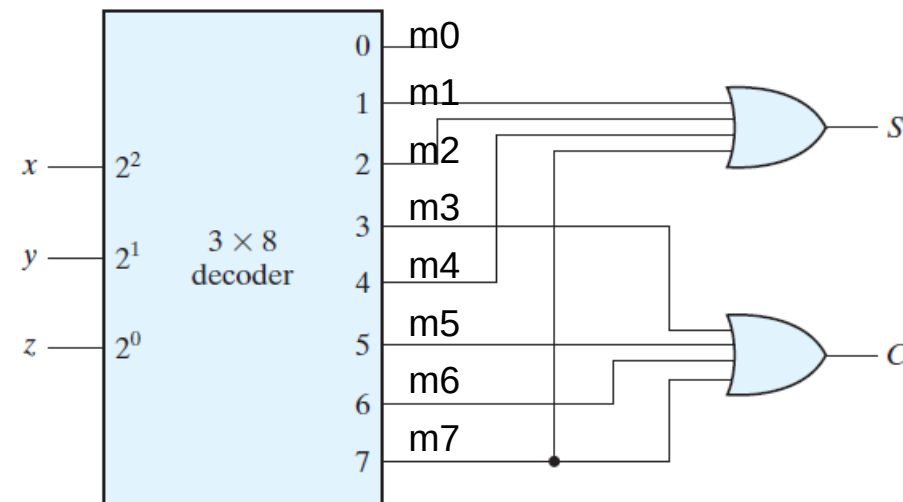


# Decoder for logic implementation

## Example2

- Exercise:
  - Implement  $Y = A \text{ XNOR } B$  using a 2-to-4 line decoder and external OR gate, you need to clearly write down the input and output pins

$$\begin{aligned} Y &= A \text{ XNOR } B \\ &= (A \oplus B)' \\ &= A'B' + AB \\ &= \sum(0, 3) \end{aligned}$$

Connect output 0 and 3  
to an OR gate

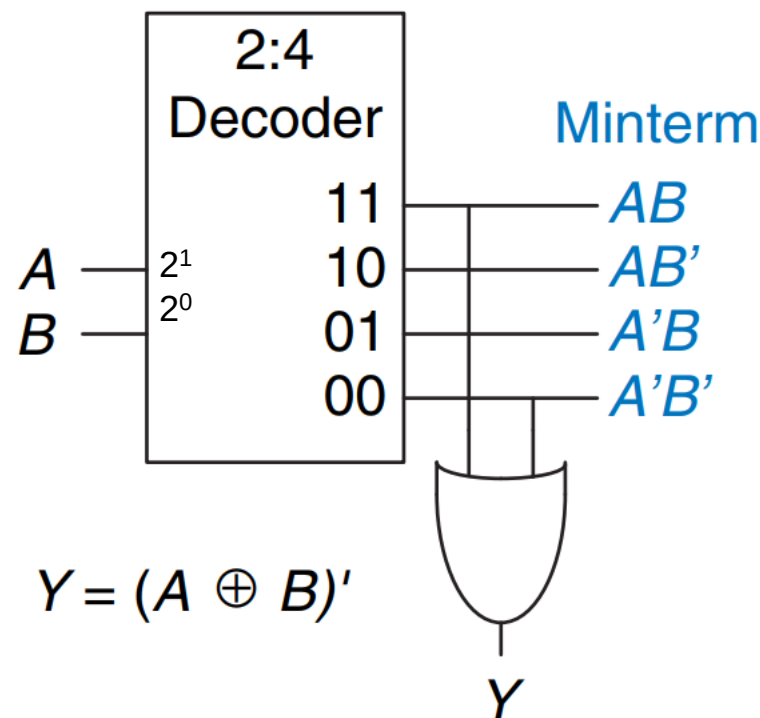

# 7400-series integrated circuits

- The 7400 series is a popular logic family integrated circuits (ICs).
- They are MSIs (Medium-scale integration)



IC 7447 BCD to 7 Segment **Decoder** Driver

Part no.: 50420

Manufacturer: **Major Brands**

Manufacturer no.: 7447


[+ Compare Product](#)

1: \$2.95

10: \$2.79

100: \$2.29

500: \$1.95

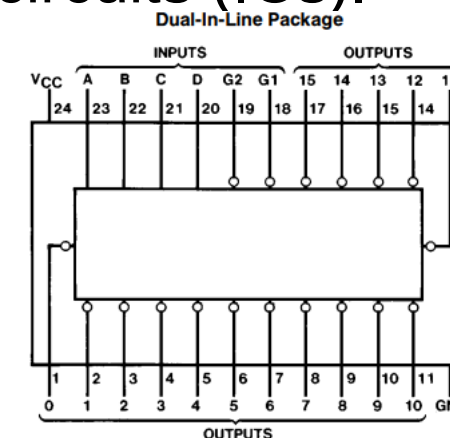

IC 74154 4-to-16 LINE **DECODER**/DEMULTIPLEXER

Part no.: 49568

Manufacturer: **Major Brands**

Manufacturer no.: 74154

[+ Compare Product](#)

1: \$5

10: \$

100:

Function Table

|    |    | Inputs |   |   |   | Outputs |   |   |   |   |   |   |   |   |   |    |    |    |    |    |    |
|----|----|--------|---|---|---|---------|---|---|---|---|---|---|---|---|---|----|----|----|----|----|----|
| G1 | G2 | D      | C | B | A | 0       | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 |
| L  | L  | L      | L | L | L | L       | H | H | H | H | H | H | H | H | H | H  | H  | H  | H  | H  | H  |
| L  | L  | L      | L | L | H | H       | H | L | H | H | H | H | H | H | H | H  | H  | H  | H  | H  | H  |
| L  | L  | L      | L | H | L | H       | H | L | H | H | H | H | H | H | H | H  | H  | H  | H  | H  | H  |
| L  | L  | L      | H | L | L | H       | H | H | L | H | H | H | H | H | H | H  | H  | H  | H  | H  | H  |
| L  | L  | L      | H | L | H | H       | H | H | H | L | H | H | H | H | H | H  | H  | H  | H  | H  | H  |
| L  | L  | L      | H | H | H | L       | H | H | H | H | L | H | H | H | H | H  | H  | H  | H  | H  | H  |
| L  | L  | L      | L | H | L | L       | L | H | H | H | H | H | H | L | H | H  | H  | H  | H  | H  | H  |
| L  | L  | L      | L | L | L | L       | H | H | H | H | H | H | H | H | H | H  | H  | H  | H  | H  | H  |
| L  | L  | L      | L | L | L | L       | H | H | H | H | H | H | H | H | H | L  | H  | H  | H  | H  | H  |
| L  | L  | L      | L | L | L | L       | H | H | H | H | H | H | H | H | H | H  | L  | H  | H  | H  | H  |
| L  | L  | L      | L | L | L | L       | H | H | H | H | H | H | H | H | H | H  | H  | L  | H  | H  | H  |
| L  | L  | L      | L | L | L | L       | H | H | H | H | H | H | H | H | H | H  | H  | H  | L  | H  | H  |
| L  | L  | L      | L | L | L | L       | H | H | H | H | H | H | H | H | H | H  | H  | H  | H  | L  | H  |
| L  | L  | L      | L | L | L | L       | H | H | H | H | H | H | H | H | H | H  | H  | H  | H  | H  | L  |
| L  | L  | L      | L | L | L | L       | H | H | H | H | H | H | H | H | H | H  | H  | H  | H  | H  | L  |
| L  | L  | L      | L | L | L | L       | H | H | H | H | H | H | H | H | H | H  | H  | H  | H  | H  | L  |
| L  | L  | L      | L | L | L | L       | H | H | H | H | H | H | H | H | H | H  | H  | H  | H  | H  | L  |
| L  | L  | L      | L | L | L | L       | H |   |   |   |   |   |   |   |   |    |    |    |    |    |    |

H = High Level, L = Low Level, X = Don't Care



IC 7442 4-LINE BCD-to-10 LINE DECIMAL **DECODER**

Part no.: 50374

Manufacturer: **Major Brands**


1: \$3

10: \$

# Decoder for logic implementation

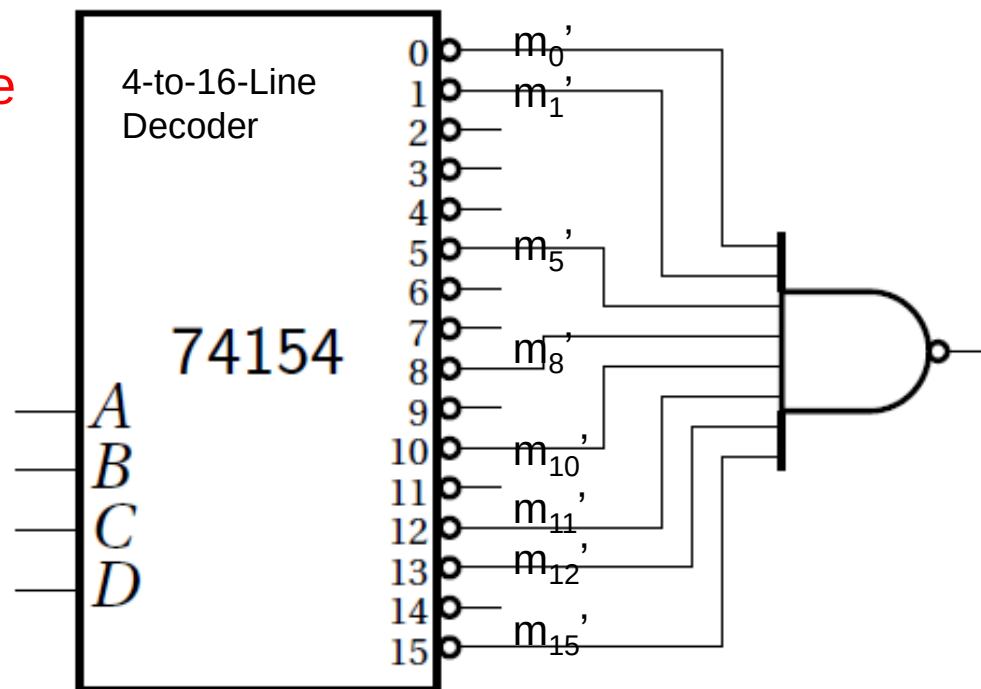
## Example3

- Using 74154 for logic function implementation
  - 74154: a 4-to-16 line decoder
  - Characteristics: If  $A = B = C = D = 0$  the output 0 of the decoder is **0** while all other outputs are 1. (**active low output**) → generate inverse of minterms
- Example:
  - $F(A,B,C,D) = \sum(0, 1, 5, 8, 10, 12, 13, 15)$ .  
 $= [(m_0 + m_1 + m_5 + m_8 + m_{10} + m_{12} + m_{13} + m_{15})']'$   
 $= (m_0' \cdot m_1' \cdot m_5' \cdot m_8' \cdot m_{10}' \cdot m_{12}' \cdot m_{13}' \cdot m_{15}')$
  - thus a nand gate is used instead of an or gate


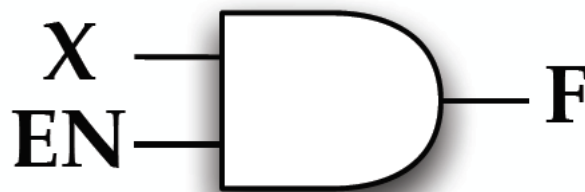
# Enabling

- Enabling permits an input signal to pass through to an output.



- $F = EN \cdot X$

| EN | X | F |
|----|---|---|
| 0  | 0 | 0 |
| 0  | 1 | 0 |
| 1  | 0 | 0 |
| 1  | 1 | 1 |




# Decoder with Enable Input

- Decoder with enable control (E)

Step1,2


|                            | E | $A_0$ | $C_1$ | $C_0$ |
|----------------------------|---|-------|-------|-------|
| Active High Enable         | 1 | 0     | 0     | 1     |
|                            | 1 | 1     | 1     | 0     |
| Low $\rightarrow$ disabled | 0 | X     | 0     | 0     |

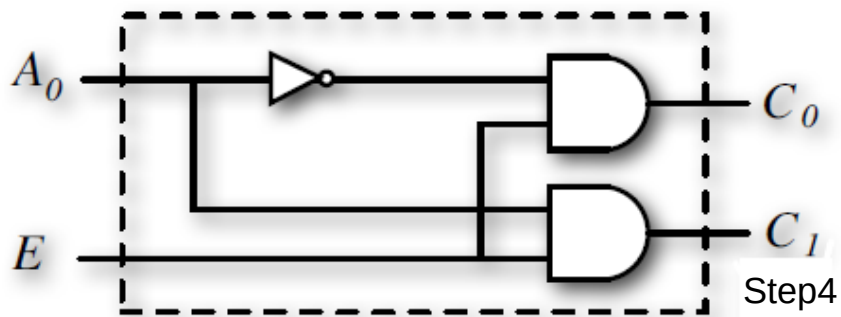

Step3

$$C_0 = EA_0'$$

$$C_1 = EA_0$$

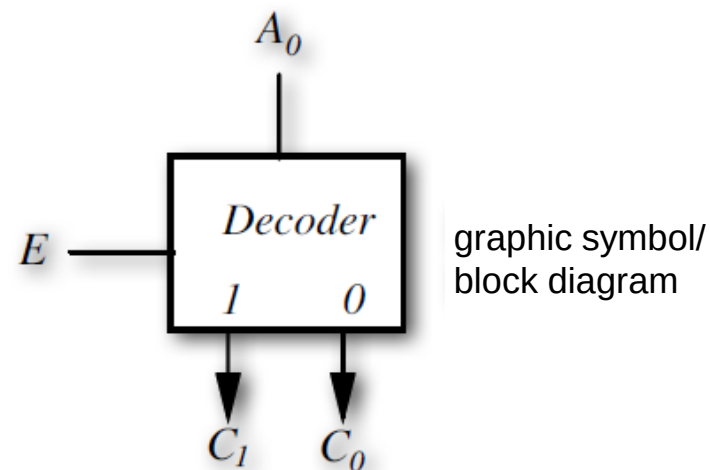


1-2 Line Decoder with Enable

# Decoder with Active-Low Enable


- If constructed with NAND gates
  - decoder minterms in their complemented form (more economical)

|                             | $E$ | $A$ | $B$ | $D_0$ | $D_1$ | $D_2$ | $D_3$ |
|-----------------------------|-----|-----|-----|-------|-------|-------|-------|
| High $\rightarrow$ disabled | 1   | X   | X   | 1     | 1     | 1     | 1     |
| Active Low Enable           | 0   | 0   | 0   | 0     | 1     | 1     | 1     |
|                             | 0   | 0   | 1   | 1     | 0     | 1     | 1     |
|                             | 0   | 1   | 0   | 1     | 1     | 0     | 1     |
|                             | 0   | 1   | 1   | 1     | 1     | 1     | 0     |

Output in complement form

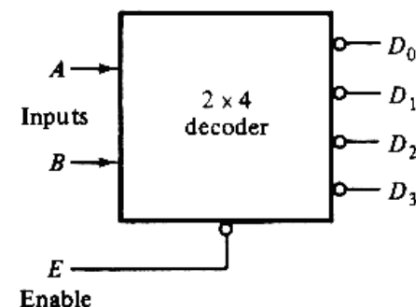

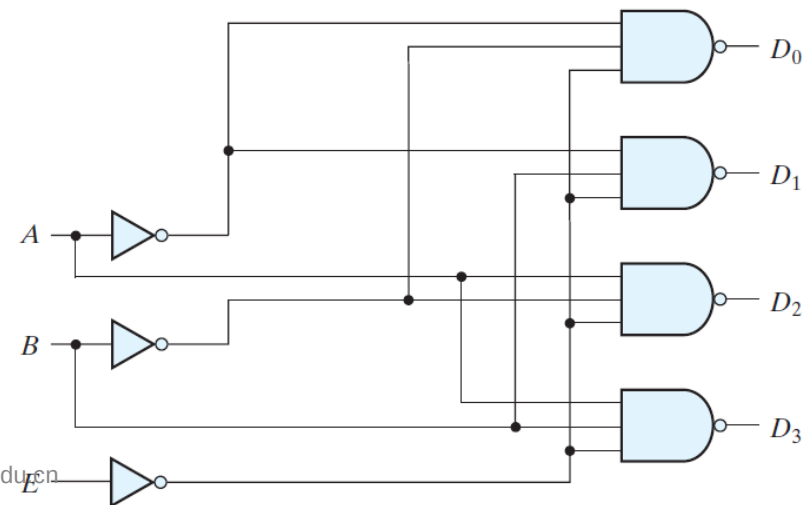
$$\begin{aligned} D_0 &= (E'A'B')' \\ D_1 &= (E'A'B)' \\ D_2 &= (E'AB')' \\ D_3 &= (E'AB)' \end{aligned}$$


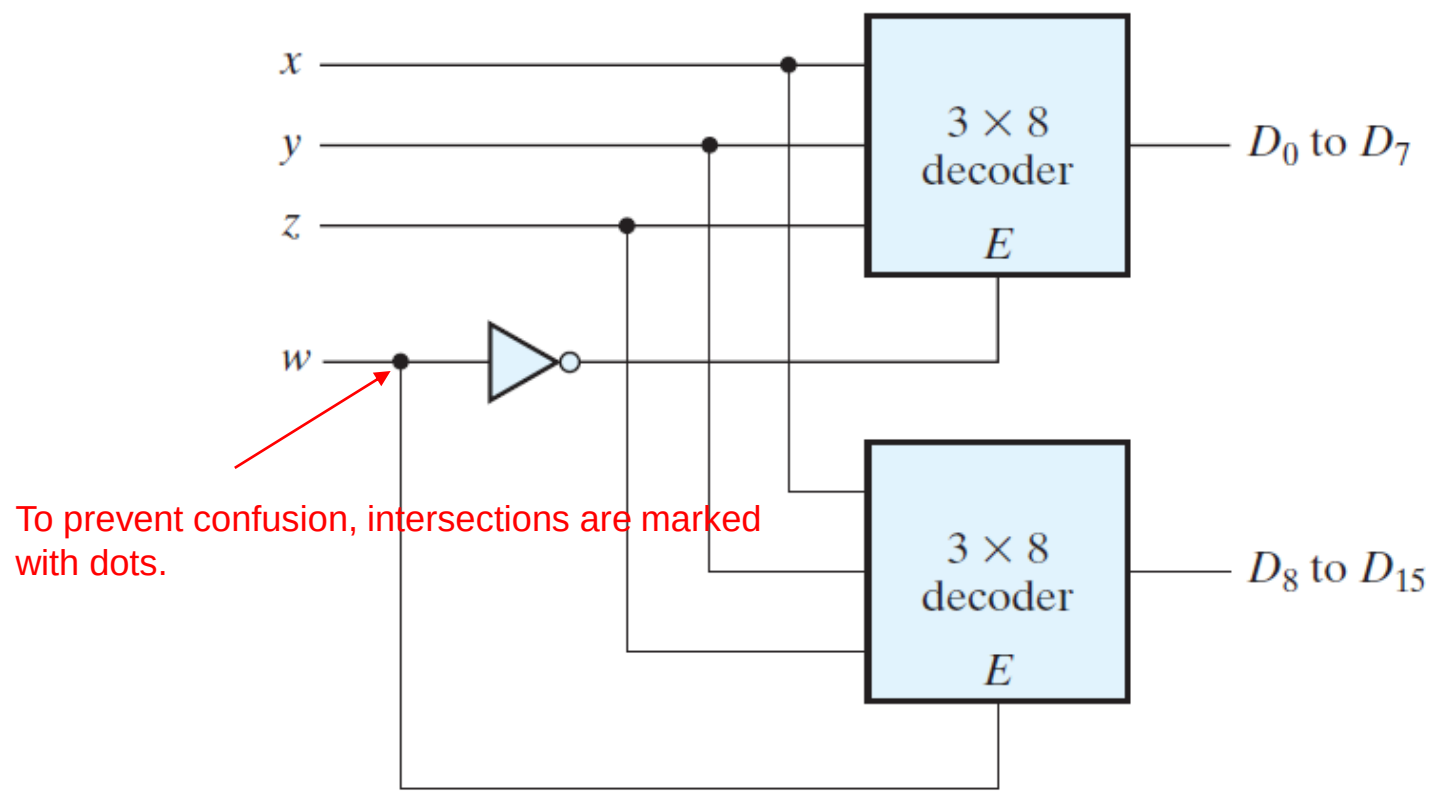
# Decoder Expansion

- Larger decoders can be implemented with smaller decoders
- Question, is this decoder's enable active high or low?





A 4-to-16-line decoder from two 3-to-8-line decoders

# Other Decoders

- BCD-to-7-Segment Display Decoder
  - input (ABCD), output (abcdefg)(MSB to LSB)
  - ABCD:0000~1001(0~9)

| BCD Input        |   |   |   | 7-Segment Display |   |   |   |   |   |   |
|------------------|---|---|---|-------------------|---|---|---|---|---|---|
| A                | B | C | D | a                 | b | c | d | e | f | g |
| 0                | 0 | 0 | 0 | 1                 | 1 | 1 | 1 | 1 | 1 | 0 |
| 0                | 0 | 0 | 1 | 0                 | 1 | 1 | 0 | 0 | 0 | 0 |
| 0                | 0 | 1 | 0 | 1                 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0                | 0 | 1 | 1 | 1                 | 1 | 1 | 0 | 0 | 1 | 1 |
| 0                | 1 | 0 | 0 | 0                 | 1 | 1 | 0 | 0 | 1 | 1 |
| 0                | 1 | 0 | 1 | 1                 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0                | 1 | 1 | 0 | 1                 | 0 | 1 | 1 | 1 | 1 | 1 |
| 0                | 1 | 1 | 1 | 1                 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1                | 0 | 0 | 0 | 1                 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1                | 0 | 0 | 1 | 1                 | 1 | 1 | 0 | 1 | 1 | 1 |
| All other inputs |   |   |   | 0                 | 0 | 0 | 0 | 0 | 0 | 0 |

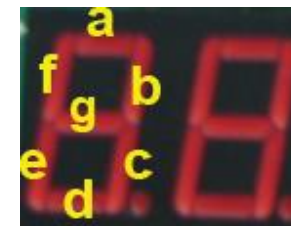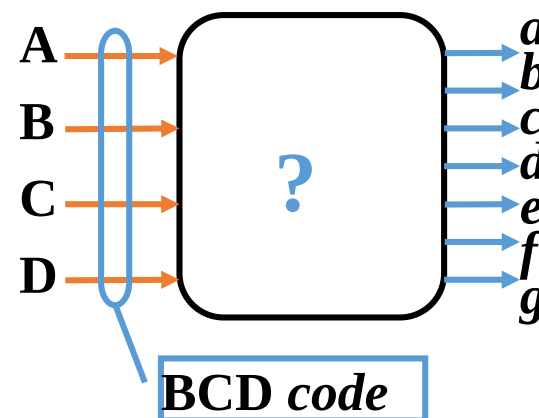


$$\begin{aligned}
 a &= A'C + A'BD + B'C'D' + A'B'C' \\
 b &= A'B' + A'C'D' + A'CD + AB'C' \\
 c &= A'B + A'D + B'C'D' + AB'C' \\
 d &= A'CD' + A'B'C + B'C'D' + AB'C' + A'BC'D \\
 e &= A'CD' + B'C'D' \\
 f &= A'BC' + A'C'D' + A'BD' + AB'C' \\
 g &= A'CD' + A'B'C + A'BC' + AB'C'
 \end{aligned}$$

# Outline



- Decoder
- **Multiplexer**
- Encoder

# Multiplexers (MUX)

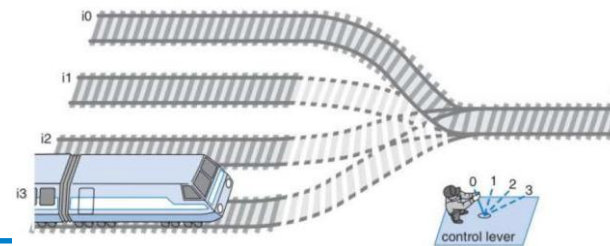

- A Multiplexer selects (usually by  $n$  select lines) binary information from one of many (usually  $2^n$ ) input lines and directs it to a single output line.

2:1 multiplexer

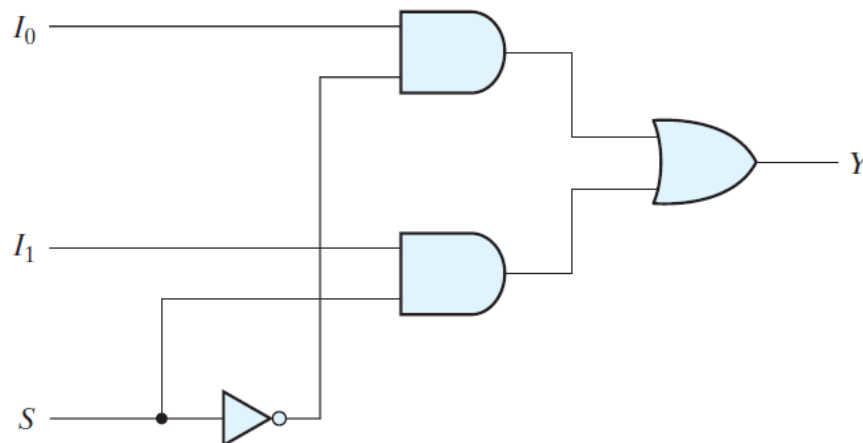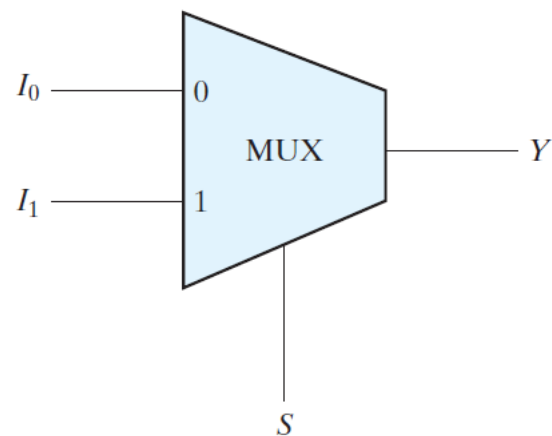

Function table


| S | Y     |
|---|-------|
| 0 | $I_0$ |
| 1 | $I_1$ |

Logic equation

$$Y = S'I_0 + SI_1$$


function table lists the input that is passed to the output for each combination of the binary selection values

# 4:1 MUX

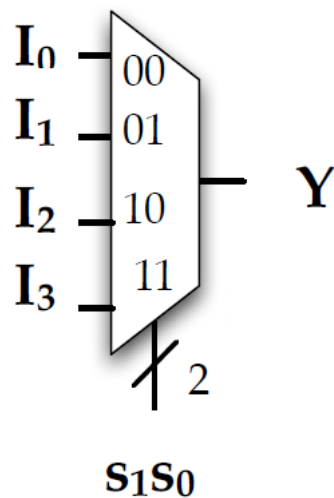

Function table

| $S_1$ | $S_0$ | $Y$   |
|-------|-------|-------|
| 0     | 0     | $I_0$ |
| 0     | 1     | $I_1$ |
| 1     | 0     | $I_2$ |
| 1     | 1     | $I_3$ |

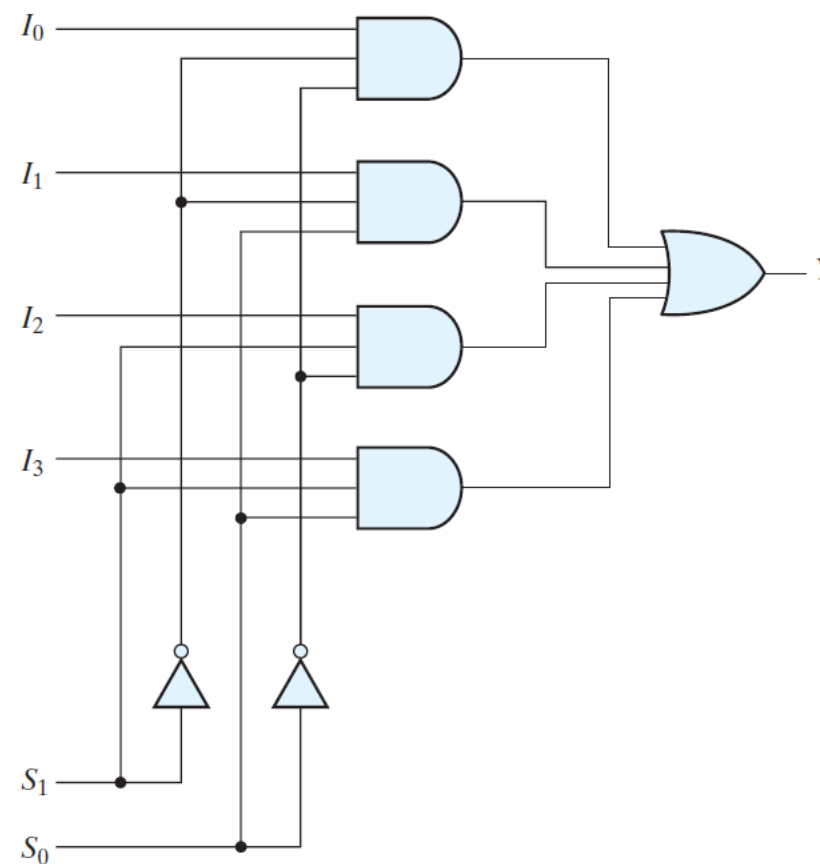


Logic equation

$$Y = s_1's_0'I_0 + s_1's_0I_1 + s_1s_0'I_2 + s_1s_0I_3$$
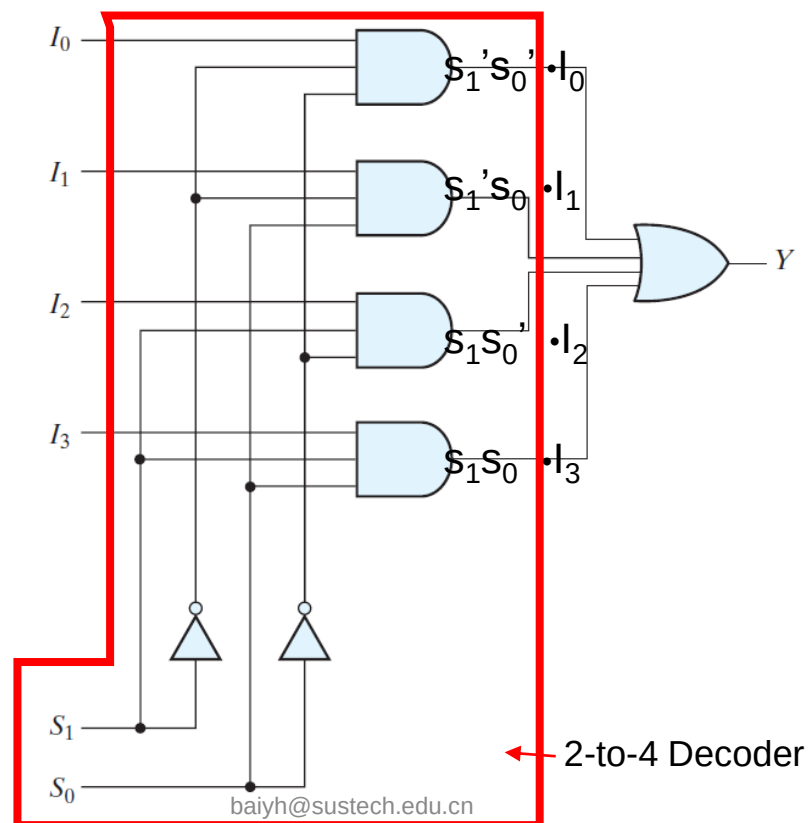
# MUX Composition

- MUX = decoder + OR gate
  - The device has two control or selection lines  $S_1$  and  $S_0$ ,
  - Logic equation:  $Y = s_1's_0'I_0 + s_1's_0I_1 + s_1s_0'I_2 + s_1s_0I_3$






# MUX for logic implementation Example1


- Implement AND function using MUX
  - can be used as a look-up table
  - 4:1 multiplexer can be used (truth table)

| A | B | Y |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

$Y = AB$

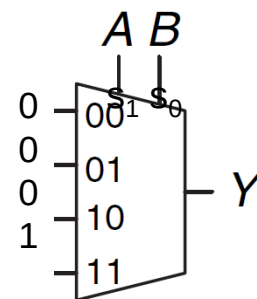

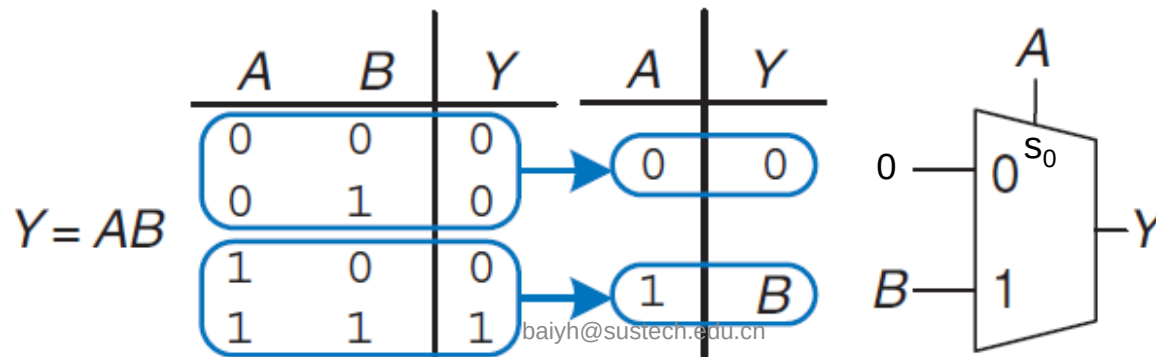- What if only 2:1 MUX is allowed to use?
  - By using variable as data inputs




# MUX Exercise

- Exercise: Implement XNOR function using
  - 1) a 4:1 MUX
  - 2) a 2:1 MUX

# MUX for logic implementation Example2



- Implement the function  $Y(A,B,C) = \sum(0,3,4,5)$  with MUX

## 1. using 8:1 MUX

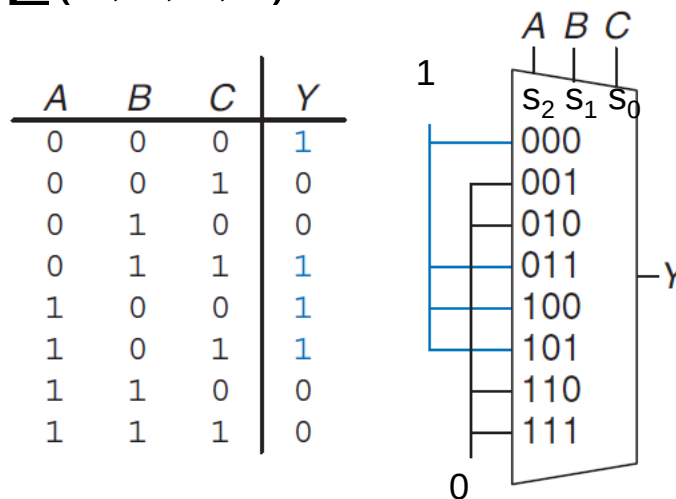
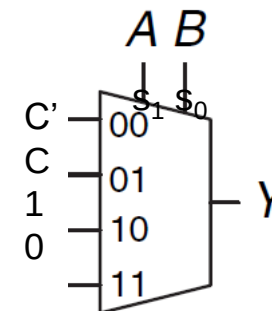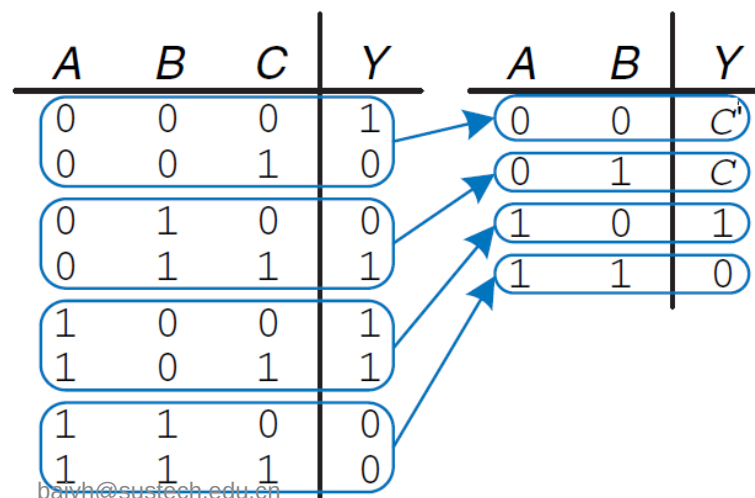
## 2. using 4:1 MUX

- We can use 4:1 MUX by reducing the truth table to four rows by letting A,B as select bit  $s_1$  and  $s_0$




# MUX for logic implementation Example2

- Implement the function  $Y(A,B,C) = \sum(0,3,4,5)$  with MUX
3. Using 2:1 MUX?

| A | B | C | Y |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |

$Y = (B \oplus C)'$


$Y = B'$

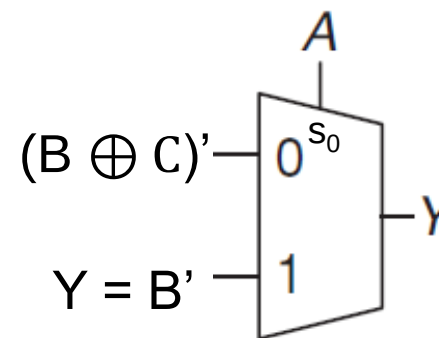

# MUX for logic implementation Example3

- Implement  $F(A, B, C, D) = (1, 3, 4, 11, 12, 13, 14, 15)$  with three selection inputs Multiplexer.
  - A must be connected to selection input  $S_2$  so that A, B, and C correspond to selection inputs  $S_2, S_1$ , and  $S_0$ , respectively


| A | B | C | D | F |          |
|---|---|---|---|---|----------|
| 0 | 0 | 0 | 0 | 0 | $F = D$  |
| 0 | 0 | 0 | 1 | 1 |          |
| 0 | 0 | 1 | 0 | 0 | $F = D$  |
| 0 | 0 | 1 | 1 | 1 |          |
| 0 | 1 | 0 | 0 | 1 | $F = D'$ |
| 0 | 1 | 0 | 1 | 0 |          |
| 0 | 1 | 1 | 0 | 0 | $F = 0$  |
| 0 | 1 | 1 | 1 | 0 |          |
| 1 | 0 | 0 | 0 | 0 | $F = 0$  |
| 1 | 0 | 0 | 1 | 0 |          |
| 1 | 0 | 1 | 0 | 0 | $F = D$  |
| 1 | 0 | 1 | 1 | 1 |          |
| 1 | 1 | 0 | 0 | 1 | $F = 1$  |
| 1 | 1 | 0 | 1 | 1 |          |
| 1 | 1 | 1 | 0 | 1 | $F = 1$  |
| 1 | 1 | 1 | 1 | 1 |          |

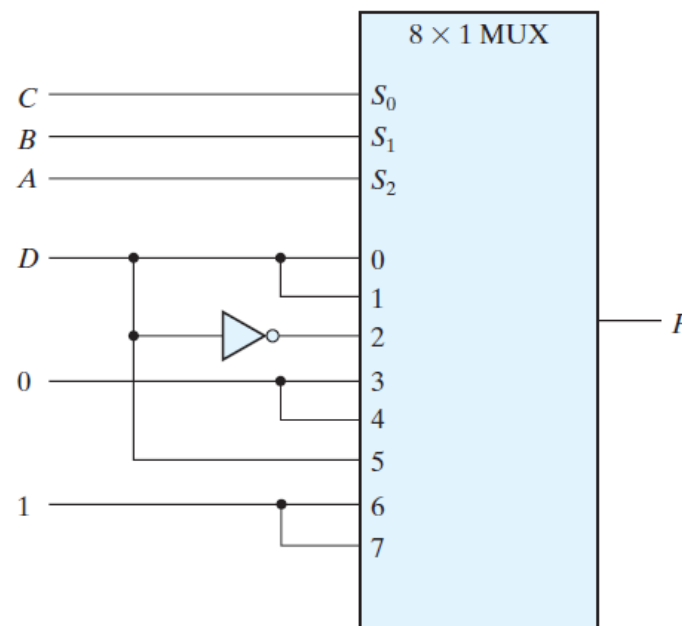


# Quadruple 2:1 MUX (4-bit 2:1 MUX)

| $E$ | $S$ | Output $Y$ |
|-----|-----|------------|
| 1   | X   | all 0's    |
| 0   | 0   | select $A$ |
| 0   | 1   | select $B$ |

Function table

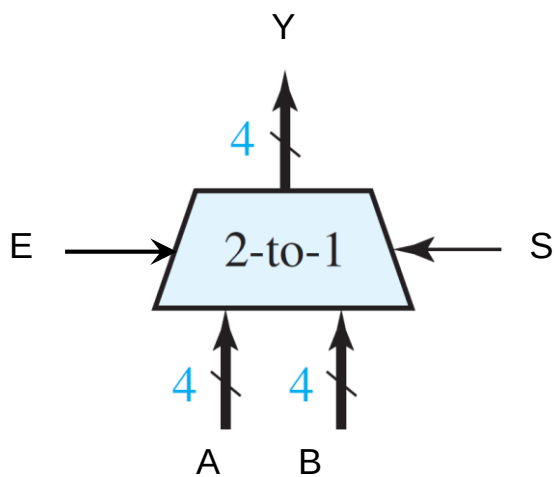

four 2:1 MUX with enable

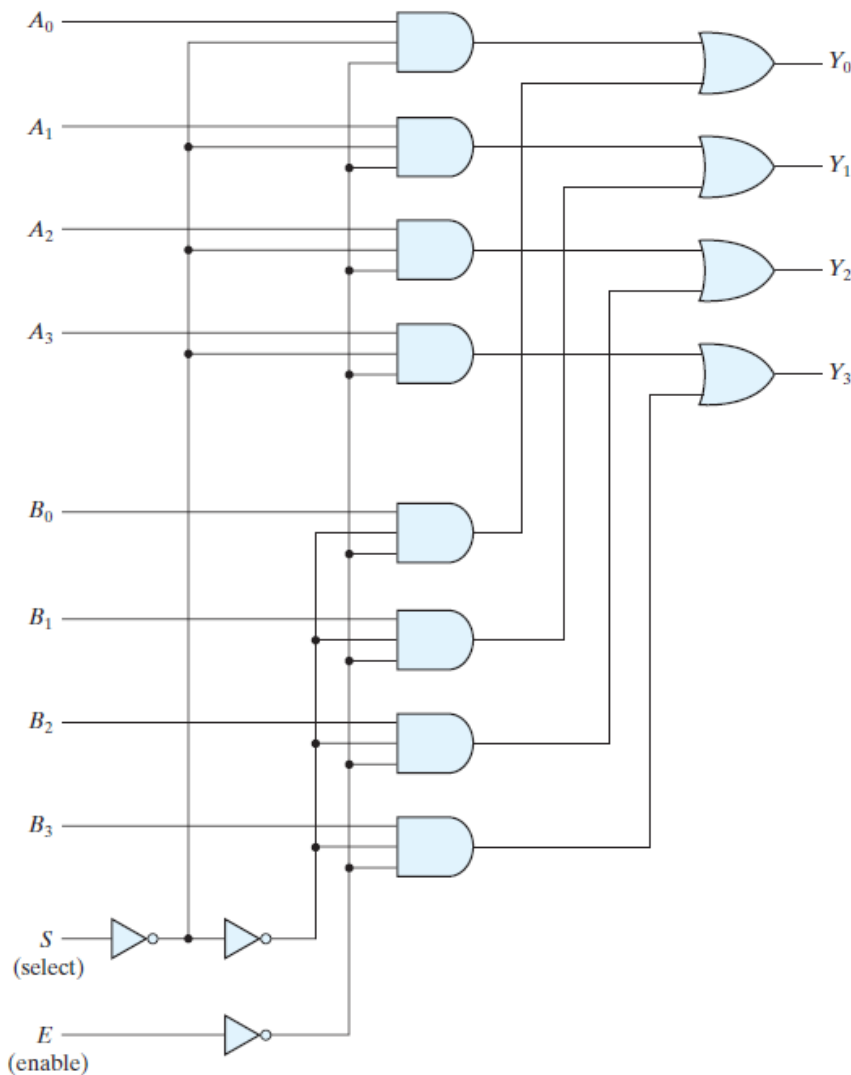

# MUX Expansion

- Wider multiplexers, such as 8:1 and 16:1 multiplexers, can be built with smaller multiplexers

Function table


| $S_1$ | $S_0$ | Y     |
|-------|-------|-------|
| 0     | 0     | $D_0$ |
| 0     | 1     | $D_1$ |
| 1     | 0     | $D_2$ |
| 1     | 1     | $D_3$ |

$f_1 = S_0'D_0 + S_0D_1$   
 $f_2 = S_0'D_2 + S_0D_3$

Logic equation

$$\begin{aligned}
 Y &= s_1'f_1 + s_1f_2 \\
 &= s_1'(s_0'D_0 + s_0D_1) + s_1(s_0'D_2 + s_0D_3) \\
 &= s_1's_0'D_0 + s_1's_0D_1 + s_1s_0'D_2 + s_1s_0D_3
 \end{aligned}$$


4:1 MUX with three 2:1 MUX

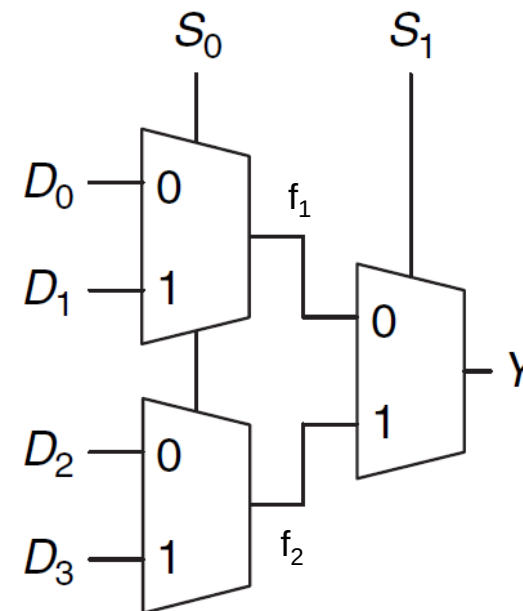

# MUX Expansion

- How to build a 16-to-1 multiplexer using
  - $16 = 2^4$
  - 4 bits for selection

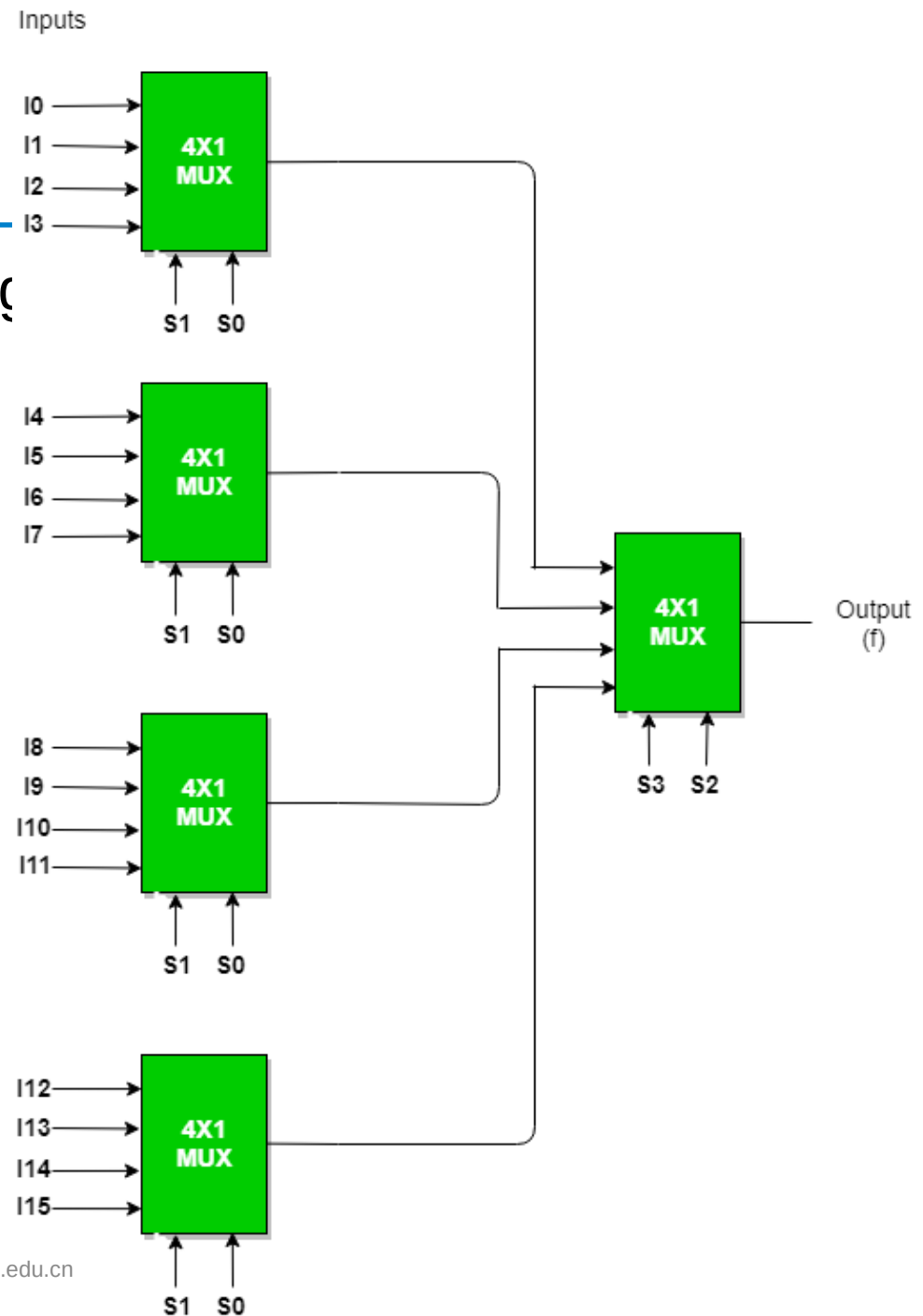Exercise: How to build a 8-to-1 multiplexer using two 4-to-1 MUX and a 2-to-1 MUX? You must carefully connect the selection and input pins






# Outline

- Decoder
- Multiplexer
- **Encoder**

# Encoder

- An encoder is an inverse of a decoder
- Encoder is a logic module that converts a **one-hot** input signal to a binary-encoded output signal
- Other input patterns are **forbidden** in the truth table
- Example: a 4-→2 encoder

| $a_3$ | $a_2$ | $a_1$ | $a_0$ | $b_1$ | $b_0$ |
|-------|-------|-------|-------|-------|-------|
| 0     | 0     | 0     | 1     | 0     | 0     |
| 0     | 0     | 1     | 0     | 0     | 1     |
| 0     | 1     | 0     | 0     | 1     | 0     |
| 1     | 0     | 0     | 0     | 1     | 1     |

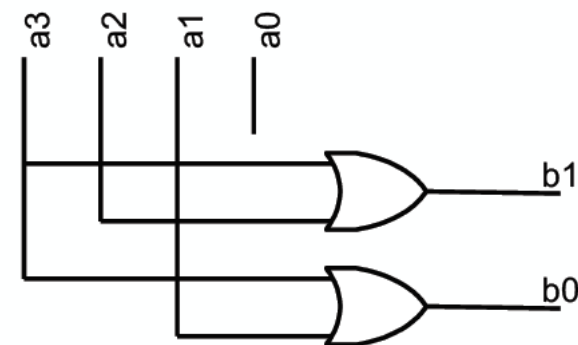

$$b_0 = a_3 + a_1$$

$$b_1 = a_3 + a_2$$

# Encoder

- A combinational logic that performs the inverse operation of a decoder
  - Only one input has value 1 at any given time
  - Can be implemented with OR gates
- However, when both D3 and D6 goes 1, the output will be 111 (ambiguity)!

illegal inputs !Use priority encoder!

| Inputs |       |       |       |       |       |       |       | Outputs |     |     |
|--------|-------|-------|-------|-------|-------|-------|-------|---------|-----|-----|
| $D_0$  | $D_1$ | $D_2$ | $D_3$ | $D_4$ | $D_5$ | $D_6$ | $D_7$ | $x$     | $y$ | $z$ |
| 1      | 0     | 0     | 0     | 0     | 0     | 0     | 0     | 0       | 0   | 0   |
| 0      | 1     | 0     | 0     | 0     | 0     | 0     | 0     | 0       | 0   | 1   |
| 0      | 0     | 1     | 0     | 0     | 0     | 0     | 0     | 0       | 1   | 0   |
| 0      | 0     | 0     | 1     | 0     | 0     | 0     | 0     | 0       | 1   | 1   |
| 0      | 0     | 0     | 0     | 1     | 0     | 0     | 0     | 1       | 0   | 0   |
| 0      | 0     | 0     | 0     | 0     | 1     | 0     | 0     | 1       | 0   | 1   |
| 0      | 0     | 0     | 0     | 0     | 0     | 1     | 0     | 1       | 1   | 0   |
| 0      | 0     | 0     | 0     | 0     | 0     | 0     | 1     | 1       | 1   | 1   |

$$x = D_4 + D_5 + D_6 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$z = D_1 + D_3 + D_5 + D_7$$

# Priority Encoder

- Ensure only one of the input is encoded
- Assuming  $D_3$  has the highest priority, while  $D_0$  has the lowest priority.
- X is the don't care conditions, V is the valid output indicator.

| Inputs |       |       |       | Outputs |     |     |
|--------|-------|-------|-------|---------|-----|-----|
| $D_0$  | $D_1$ | $D_2$ | $D_3$ | $x$     | $y$ | $V$ |
| 0      | 0     | 0     | 0     | X       | X   | 0   |
| 1      | 0     | 0     | 0     | 0       | 0   | 1   |
| X      | 1     | 0     | 0     | 0       | 1   | 1   |
| X      | X     | 1     | 0     | 1       | 0   | 1   |
| X      | X     | X     | 1     | 1       | 1   | 1   |

$$V = D_0 + D_1 + D_2 + D_3$$

# Priority Encoder

| $D_0D_1$ |    | $D_2D_3$   |               |               |               |
|----------|----|------------|---------------|---------------|---------------|
|          |    | 00         | 01            | 11            | 10            |
| $D_0$    | 00 | $m_0$<br>X | $m_1$<br>1    | $m_3$<br>1    | $m_2$<br>1    |
|          | 01 | $m_4$      | $m_5$<br>1    | $m_7$<br>1    | $m_6$<br>1    |
|          | 11 | $m_{12}$   | $m_{13}$<br>1 | $m_{15}$<br>1 | $m_{14}$<br>1 |
|          | 10 | $m_8$      | $m_9$<br>1    | $m_{11}$<br>1 | $m_{10}$<br>1 |

$x = D_2 + D_3$

$$x = D_2 + D_3$$

$$y = D_3 + D_1 D_2'$$

$$V = D_0 + D_1 + D_2 + D_3$$

| $D_0D_1$ |    | $D_2D_3$      |               |               |          |
|----------|----|---------------|---------------|---------------|----------|
|          |    | 00            | 01            | 11            | 10       |
| $D_0$    | 00 | $m_0$<br>X    | $m_1$<br>1    | $m_3$<br>1    | $m_2$    |
|          | 01 | $m_4$<br>1    | $m_5$<br>1    | $m_7$<br>1    | $m_6$    |
|          | 11 | $m_{12}$<br>1 | $m_{13}$<br>1 | $m_{15}$<br>1 | $m_{14}$ |
|          | 10 | $m_8$         | $m_9$<br>1    | $m_{11}$<br>1 | $m_{10}$ |

$y = D_3 + D_1 D_2'$

