

DIGITAL LOGIC

Chapter 5 part1: Latches and Flip-flops

2025 Fall

This PowerPoint is for internal use only at Southern University of Science and Technology.
Please do not repost it on other platforms without permission from the instructor.

Today's Agenda


- Recap
- Context
 - Latches
 - Flip-Flops
- Reading: Textbook, Chapter 5.1-5.4

Recap

- Decoder: Converts n -bit input to 2^n unique outputs (one-hot); acts as a minterm generator
 - One-Hot Encoding: Represents N states with N bits; only one bit is active at a time
 - Decoder Uses:
 - Minterm generation
 - Data demultiplexing
 - Address & display decoding
 - Decoder with Enable: Controls operation; active-high or active-low enable inputs
 - Decoder Expansion: Larger decoders built from smaller ones
- Multiplexer (MUX): Selects one of 2^n inputs to a single output using n select lines
 - MUX for Logic Implementation: Can implement any Boolean function
 - MUX Expansion: Larger MUX built from smaller ones
- Encoder: Inverse of decoder; converts one-hot input to binary code
 - Priority Encoder: Resolves multiple active inputs by assigning priority
- Standard ICs: 7400-series MSI components widely used in practice

Sequential Circuits

 - A sequential circuit consists of a combinational circuit to which storage elements are connected to form a feedback path.
 - The binary information stored in the memory elements at any given time defines the state of the sequential circuit.
 - (inputs, current state) $\Rightarrow$ (outputs, next state)– The behavior is specified by a time sequence of inputs and internal states.






Synchronous vs. Asynchronous Sequential Circuits

- Sequential circuits are broadly classified into two main categories depending on the timing of their signals.
 - **Synchronous sequential circuit** (同步时序电路): A system whose behavior can be defined from the knowledge of its signals at discrete instants of time.
 - **Asynchronous sequential circuit** (异步时序电路): A system whose behavior depends upon input signals at any instant of time and the order in which the inputs change.
- Asynchronous circuit properties
 - Commonly used storage devices are time-delay devices, and the propagation delay of the logic gates (time-delay devices) provides the required storage.
 - Can be viewed as combinational circuit with feedback—May unstable at times

Synchronous Sequential Circuits with Clock

   - Synchronization usually is achieved by a timing device: clock generator.
 - The outputs are affected only with the application of a clock pulse.
- Clock generator generates a periodic train of clock pulses distributed throughout the system to trigger the memory elements



Storage Elements



- Some definitions:
 - State: all the information about a circuit necessary to explain its future behavior
 - Latches and flip-flops: state elements that store one bit of state
 - SR Latch (SR锁存器)
 - D Latch (D锁存器)
 - D Flip-flop (DFF, D触发器)

Outline

- Latches
- FlipFlops

SR (Set/Reset) Latch

  - Latch is an asynchronous sequential circuit (state changes whenever inputs change).
- SR latch is a basic memory element which can store one bit of information
 - Consists of two cross-coupled NOR gates or two cross-coupled NAND gates
 - Two input signals: set (S)/reset(R)
 - Two output signals: Q/Q'
 - Two useful states: set state ($Q=1, Q'=0$)/reset state ($Q=0, Q'=1$)



Basic SR Latch with NOR Gate

- Consider the four possible cases:


1. $S = 1, R = 0$
2. $S = 0, R = 1$
3. $S = 0, R = 0$
4. $S = 1, R = 1$

- 1. $S = 1, R = 0$:

- then $Q = 1$ and $Q' = 0$
- Set the output

 - 2. $S = 0, R = 1$:

- then $Q = 0$ and $Q' = 1$
- Reset the output



Basic SR Latch with NOR Gate

- Consider the four possible cases:



1. $S = 1, R = 0$
2. $S = 0, R = 1$
3. $S = 0, R = 0$
4. $S = 1, R = 1$

- 3. $S = 0, R = 0$:

- then $Q = Q_{prev}$
- **Memory!**

  - 4. $S = 1, R = 1$:


- then $Q = 0$ and $Q' = 0$
- **Invalid State!**
- **$Q' \neq \text{NOT } Q$**



Function Table of SR Latch

- SR Latch's functionality:
 - S is active $\rightarrow$ Set
 - R is active $\rightarrow$ Reset
 - S,R are inactive $\rightarrow$ Memory
 - S,R are active $\rightarrow$ Forbidden

 (S,R) must go back to (0,0) before any other change to avoid the occurrence of the undefined state




S	R	Q	Q'	
0	0	last Q	last Q'	no change
0	1	0	1	reset state
1	0	1	0	set state
1	1	0	0	forbidden

Function table


S'R' Latch with NAND Gates

• Low Active Set/Reset inputs

 - S is active $\rightarrow$ Set
- R is active $\rightarrow$ Reset
- S,R are inactive $\rightarrow$ Memory
- S,R are active $\rightarrow$ Forbidden



S	R	Q	Q'	
0	0	1	1	forbidden
0	1	1	0	set state
1	0	0	1	reset state
1	1	last Q	last Q'	no change

 


graphic symbol or S'R' Latch


Clocked SR Latch

- Use Clock (or En) to enable/disable the SR latch
 - $C=0$, no change (disabled)
 - $C=1$, operates as normal SR latch (enabled)
- Level sensitive SR Latch
 - However, undefined state when $C = S = R = 1$
- Question:
 - draw the detailed logic diagram of SR latch
 - if AND gate is changed to NAND, how about the SR latch?

C	S	R	Q	Q'	
0	X	X	last Q	last Q'	no change
1	0	0	last Q	last Q'	no change
1	0	1	0	1	reset state
1	1	0	1	0	set state
1	1	1	0	0	forbidden

 


logic diagram

 


graphic symbol

D Latch

 - D latch's inputs: Clk(En), D (only one data input)
 - Clk(En): controls when the output changes
 - D (the data input): controls what the output changes to
 - Constructed from a gated SR latch by connecting the D input to S input and D' to R.
 - Avoiding undesirable condition ($S=R=1$)



D Latch symbols

 


This make sure
S and R differs

C	D	Q	Q'	
0	X	last Q	last Q'	no change
1	0	0	1	Q follows D
1	1	1	0	Q follows D

D Latch




- D latch is also called Transparent Latch
- Level sensitive D Latch
 - When CLK = 1,
 - D passes through to Q (transparent)
 - When CLK = 0,
 - Q holds its previous value (opaque)
 - Can avoid invalid case when
 - $Q' \neq \text{NOT } Q$

C	D	Q	Q'	
0	X	last Q	last Q'	no change
1	0	0	1	Q follows D
1	1	1	0	Q follows D

 


Latch Summary

   - SR Latch with NOR gate (SR)
 - Set: Make the output 1
($S = 1, R = 0, Q = 1$)
 - Reset: Make the output 0
($S = 0, R = 1, Q = 0$)
 - Memory: $S=R=0$
- S'R' Latch with NAND gate (S'R')
 - Set: Make the output 1
($S = 0, R = 1, Q = 1$)
 - Reset: Make the output 0
($S = 1, R = 0, Q = 0$)
 - Memory: $S=R=1$
- D Latch (D)
 - Make D passes through to Q



Latches Pros and Cons

 
- A latch is enabled whenever $C=1$. (level-sensitive)
 - At any point during $C=1$, any input changes will propagate to the output (with some small delay)




- Pros
 - Useful for level-sensitive applications
 - Latches are faster because they have fewer gates and less delay.
 - Latches are simpler which means they require less hardware to implement and consume less power.

Latches Pros and Cons

 
- A latch is enabled whenever $C=1$. (level-sensitive)
 - At any point during $C=1$, any input changes will propagate to the output (with some small delay)
- Cons
 - Difficult to retain value
 - Causing erroneous shifting



 Unable to shift Q_2 and Q_3 with clock cycles delay



baiyh@sustech.edu.cn

 

Outline

- Latches
- **FlipFlops**

Flip-Flops (FF)

- Latch or Flip-Flop(FF) state changes by a control input.
 - The event is called trigger.
- A Flip-Flop is a more advanced storage element, typically constructed using two D latches or more complex circuitry.
- Example: D Flip Flop
 - Inputs: CLK, D
 - For a Positive-edge triggered D Flip Flop:
 - Samples D on rising edge of CLK
 - When CLK rises from 0 to 1, D passes through to Q
 - Otherwise, Q holds its previous value
 - Q changes only on rising edge of CLK

Trigger

- Trigger
 - The state of a latch or flip-flop is switched by a change of the control input
- Level sensitive (level-triggered) (latches)
 - The state transition starts as soon as the clock is during logic 1 (positive level-sensitive) or logic 0 (negative level-sensitive) level
- Edge-triggered (flip-flops)
 - The state transition starts only at positive (positive edge-triggered) or negative edge (negative edge-triggered) of the clock signal



(a) Response to positive level




(b) Positive-edge response



Level-Sensitive vs. Edge-Triggered



(a) Response to positive level

 


(b) Positive-edge response

  


DFF Structure

- A D flip-flop is formed by two separate latches
 - A master D latch (negative level sensitive)
 - A slave D latch (positive level sensitive)
- Positive-edge-triggered D flip-flop
 - When $\text{CLK} = 0$
 - master is transparent
 - slave is opaque
 - D passes through to Y
 - When $\text{CLK} = 1$
 - master is opaque
 - slave is transparent
 - Y passes through to Q
 - Thus, on the rising edge of the clock (CLK rises from $0 \rightarrow 1$)
 - D passes through to Q

 


Function Table of DFF


- Function table

 

C	D	Q	Q'	
0	X	last Q	last Q'	no change
1	X	last Q	last Q'	no change
$\uparrow$	0	0	1	Q follows D
$\uparrow$	1	1	0	Q follows D

 

(a) Positive-edge

 


(a) Negative-edge

D Flip-Flop Symbols

 
Question: How to design
Negative-edge-triggered
flip-flop (refer to textbook)

Timing Graph of DFF

- Positive-edge-triggered DFF
 - Q stays stable between two rising edges of the clock signal





C	D	Q	Q'	
0	X	last Q	last Q'	no change
1	X	last Q	last Q'	no change
$\uparrow$	0	0	1	Q follows D
$\uparrow$	1	1	0	Q follows D

 


Flip-flop and Latch Comparison

  - Apply the D and CLK inputs to a D latch and a D flip-flop, determine the output, Q, of each device.





Shifting


 
- Remember we wanted to shift input with clock cycles delay, but latches didn't work out



  
Unable to shift Q_2 and Q_3 with clock cycles delay



  - Now we can use FlipFlops (see next page's timing graph)



DFF with three SR Latches

 


Positive-edge-triggered D flip-flop

DFF with Asynchronous Reset


- Active low reset
 - Reset = 0: Q is forced to 0
 - Reset = 1: flip-flop behaves as ordinary D flip-flop

Function table

R	C	D	Q	Q'	
0	X	X	0	1	power on reset
1	$\uparrow$	0	0	1	Q follows D
1	$\uparrow$	1	1	0	Q follows D

 


(b) Graphic symbol

 


DFF with Reset

 - The state of FFs are unknown when power is on. A direct input can force the FFs to a known state before the system starts.
 - E.g. when Reset = 1, FF's output is forced to 0
- Synchronous vs. asynchronous resettable Flip Flop
 - Asynchronous: resets immediately when Reset = 1
 - Synchronous: resets at the clock edge only



Types of Flip-Flops

 - Flip-flops are more suitable for synchronous sequential circuits and are often used as the basic memory elements, since they only respond to a transition on a clock input.
- Other types of flip-flops can be constructed by using the DFF and external logic.
- Major FFs
 - D(data), JK, T (toggle) FFs
 - Assume only positive-edge-triggered FFs, block diagram are as follow



Characteristic Table

- **Characteristic table:** describe the behavior of a flip-flop based on its input and current state $Q(t)$ just before the rising edge of the clock, and the resulting next state $Q(t+1)$ after the clock transition.

Function table

Clk	D	Q	Q'	
0	X	last Q	last Q'	no change
1	X	last Q	last Q'	no change
$\uparrow$	0	0	1	Q follows D
$\uparrow$	1	1	0	Q follows D

Characteristic
table of DFF



D Flip-Flop Characteristic table

D	Q(t + 1)
0	0 Reset
1	1 Set

- **Characteristic equation:** derived from the characteristic table
 - e.g. Characteristic equation of DFF:

$$Q_{t+1} = D$$

J-K Flip-Flop

- e.g. Positive edge-triggered JKFF

- At rising edge of clock


- $J = K = 0$, Q is unchanged
 - $J = K = 1$, Q toggles
 - $J = 1, K = 0$, Q is set to 1
 - $J = 0, K = 1$, Q is reset to 0

- At level of clock

- Q is unchanged

Function Table

Clk	J	K	Q	Q'
0	x	x	last Q	last Q'
1	x	x	last Q	last Q'
	0	0	last Q	last Q'
	0	1	0	1
	1	0	1	0
	1	1	last Q'	last Q

 

- Characteristic equation of JKFF?

J-K Flip-Flop

Characteristic table

JK Flip-Flop			
J	K	Q(t + 1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

1. Derive the Truth table



J	K	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Characteristic equation of JKFF

$$Q(t+1) = JQ(t)' + K'Q(t)$$

• 2a. Algebraically:

$$Q(t+1)$$

$$= J'K'Q(t) + J'K \cdot 0 + JK' \cdot 1 + JKQ(t)'$$

$$= J'K'Q(t) + JK' + JKQ(t)'$$

$$= J'K'Q(t) + JK'Q(t) + JK'Q(t)' + JKQ(t)'$$



$$= JQ(t)' + K'Q(t)$$

• 2b. K-Map

		k			
		Q(t)			
J	kQ(t)	00	01	11	10
		m ₀	m ₁	m ₃	m ₂
0		0	1	0	0
1		1	1	0	1


J-K Flip-Flop

  - Graphic symbol
- can be implemented using DFF
 - Because in DFF, $Q_{t+1} = D$
 - Thus, according to JKFF's characteristic equation, $Q(t+1) = JQ(t)' + K'Q(t)$, we can derive $D = JQ(t)' + K'Q(t)$



T Flip-Flop

 - T: Toggle
 - $T = 0$, a clock edge does not change the output.
 - $T = 1$, a clock edge complements the output.
 - useful for designing binary counters.



T Flip-Flop characteristic table

T	$Q(t + 1)$
0	$Q(t)$ No change
1	$Q'(t)$ Complement



T	$Q(t)$	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

Characteristic equation of TFF

$$Q(t+1) = T'Q(t) + TQ(t)'$$

$$= T \oplus Q(t)$$



T Flip-Flop

- Graphic symbol
 - can be implemented using DFF or JKFF

Characteristic equation of TFF

$$Q(t+1) = T'Q(t) + TQ(t)'$$

$$= T \oplus Q(t)$$

  

$$Q(t+1) = JQ(t)' + K'Q(t)$$

By considering $J = K = T$