

Digital Logic


Lab7 synchronous sequential circuit - Latch, FlipFlop

Lab7

- Synchronous sequential circuit
 - Latch
 - Flip Flops (key point of lab7)
- Verilog
 - `always@(posedge clk)` , `always@(negedge clk)` vs `always@*`
 - blocking assignment vs non-blocking assignment
- Practice

Recall: 4-2 priority-en-coder

 
```
//4-2 priority-encoder
module pri_encoder(
input I0, I1, I2, I3,
output reg [1:0] Y
);
always @* begin
    casex( {I3, I2, I1, I0} )
        4'bxxx0: Y=2'b00;
        4'bxxx01: Y=2'b01;
        4'bx011: Y=2'b10;
        4'b0111: Y=2'b11;
    endcase
end
endmodule
```



If there is no 'default' branch and the branch(e.g. 4'b1111 in this demo) is not list in the branches of the 'case', the circuit state will remain unchanged, and then a **latch** will be generated to save the state.

Latch

 
- The schematic on the right hand is the schematic of the synthesized design generated by vivado.
- LDCE**: transparent Data **Latch** with Asynchronous Clear and Gate Enable



For more information on LDCE, please refer to *Xilinx 7 Series FPGA Libraries Guide for Schematic Design*

D Latch

 - Latch: the simplest binary memory elements, static device composed of gates. When the input changes, the output changes immediately.



(a) Logic diagram

En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

(b) Function table

```


module D_Latch(
input En, D,
output reg Q,
output wire nQ
);
    assign nQ = ~Q;
    always @*
        if(En)
            Q = D;
        else
            Q = Q;
endmodule

```


D Latch

- Schematic of RTL analysis:

<i>En</i>	<i>D</i>	Next state of <i>Q</i>
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

 

- Simulation result of D Latch

 

Flip Flop (design)

- The storage elements (memory) used in clocked sequential circuits are called **flipflops**.
- The most economical and efficient flip-flop constructed is the edge-triggered **D flipflop**, because it requires the smallest number of gates.


 


Figure for master-slave **positive-edge** triggered **D flip-flop**

```
module D_ff_p_from_latch(  
    input clk, D,  
    output Q  
);  
    /*module D_latch( input En,D,  
        output reg Q, output nQ );*/  
    wire P, nq_master, nq_slaver;  
    D_latch ud_master(~clk, D, P,nq_master);  
    D_latch ud_slaver(clk, P, Q, nq_slaver);  
endmodule
```

Flip Flop (testbench, waveform)

 master-slave **positive-edge** triggered D flip-flop



```
module D_ff_p_from_latch(
input clk, D,
output Q
);
/*module D_latch( input En,D,
output reg Q, output nQ );*/
wire P, nq_master, nq_slaver;
D_latch ud_master(~clk, D, P,nq_master);
D_latch ud_slaver(clk, P, Q, nq_slaver);
endmodule
```




```
module D_ff_p_tb( );
/*module D_ff_p_from_latch(input clk, D, output Q ); */
reg sclk, sD;
wire sQ;
D_ff_p_from_latch dut1(sclk, sD, sQ);
initial begin
sclk=1'b0;
forever #10 sclk = ~sclk;
end
initial fork
sD = 1'b0;
#15 sD = 1'b1;
#35 sD = 1'b0;
#60 $finish;
join
endmodule
```


D Flip Flop

$$Q^{n+1} = D$$

Clk	Q
↑	D
0	no change
1	no change
↓	no change

 Here is **positive-edge** triggered D flip-flop



```

module D_flipflop(
    input clk, D,
    output reg Q,
    output nQ
);
    always @(posedge clk)
        Q <= D;
    assign nQ = ~Q;
endmodule


```

Name	Value
sclk	1
sD	0
sQ	0
snQ	1



Practice(1)

 - Implement a negative-edge triggered D flipflop
 - a) by using two D latch
 - b) using behavior manner
- Build a testbench to test the negative-edge triggered D flipflop, do the simulation.
 - the expected waveform of the negative-edge triggered D flipflop is shown in the following figure.




JK Flip Flop(1)


- $Q^{n+1} = J\bar{Q}^n + \bar{K}Q^n$

JK		00	01	11	10
Q ⁿ	0	0	0	1	1
	1	1	0	0	1

J	K	Q ⁿ⁺¹
0	0	no change
0	1	0
1	0	1
1	1	Q ^{n'}

 

(a) Circuit diagram

 

(b) Graphic symbol

JK Flip flop(2)

```

module J_K_Flip_Flop(
    input Clk, J, K,
    output reg Q,
    output nQ
);
    assign nQ = ~Q;
    always @ (posedge Clk)
        case ({J, K})
            2'b10: Q<= 1'b1; //set
            2'b01: Q<= 1'b0; //reset
            2'b11: Q<= nQ; //reverse
            2'b00: Q<= Q; //keep
        endcase
endmodule

```

$$Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$$

J	K	Q^{n+1}
0	0	no change
0	1	0
1	0	1
1	1	Q^n



Using jk flip flop to implement D flip flop

- JK Flip-Flop: $Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$
- D Flip-Flop: $Q^{n+1} = D = D\overline{Q}^n + DQ^n$


J	K	Q^{n+1}
0	0	no change
0	1	0
1	0	1
1	1	Q^n

Clk	Q
↑	D
0	no change
1	no change
↓	no change

```


module Dff_byJKff(
  input clk, D,
  output Q, nQ
);
  J_K_Flip_Flop u(clk, D, ~D, Q, nQ);
endmodule

```

 

T Flip Flop

 - The T (toggle) flip-flop is a complementing flip-flop.




T	Q^{n+1}
0	Q^n
1	$\sim Q^n$

```
module T_Flip_Flop(  
    input Clk, T,  
    output reg Q,  
    output nQ  
);  
    assign nQ = ~Q;  
    always @(posedge Clk)  
        case(T)  
            1'b1: Q<= ~Q;  
            1'b0: Q<= Q;  
        endcase  
endmodule
```

Using jk flip flop to implement T flip flop

 - The T (toggle) can be obtained from a JK flip-flop when inputs J and K are tied together.




(a) From JK flip-flop

T	Q^{n+1}
0	Q^n
1	$\sim Q^n$

J	K	Q^{n+1}
0	0	no change
0	1	0
1	0	1
1	1	Q^n
 
```
module Tff_by_JKff(
    input Clk, T,
    output Q, nQ
);
    J_K_Flip_Flop uT( Clk, T, T, Q, nQ);
endmodule
```



Recall: Wire Vs Reg

- There are two data types in Verilog: **wire** and **register**.
 - **wire** is a kind of net, which is equivalent to physical connection.
 - **wire** is used to connects two points, and thus does **not have any driving strength**
 - **wire** data types can be used for connecting the output port to the actual driver
 - a **wire** can be assigned a value by a continuous assign statement, which is used for **designing combinational logic**
 - **default data type is wire**: this means that if you declare a port or variable without specifying reg or wire, it will be a 1-bit wide wire.
 - **reg** is a kind of register, which is equivalent to memory cell.
 - **reg** can **store value and drive strength**. **Reg** can be used for **modeling both combinational and sequential logic**.
 - **reg** data type can be driven from initial and always block.
 - **The LHS of a behavioral block(initial , always) should be declared as reg**
 - **input port** could drive by both wire/register, but it could ONLY be declared as wire
 - **output port** can be declared as wire or register, but it can ONLY drive wire
 - bidirectional port can only be declared as wire

http://www.asic-world.com/tidbits/wire_reg.html

Verilog Assignment

- Continuous Assignment (Data flow Design)
- Procedural Assignment (Behavioral Design)
 - Blocking Assignment '='
 - Nonblocking Assignment '<='

Verilog Assignments

- Continuous Assignment (Dataflow Design)
 - LHS must be wire
- Procedural Assignment (Behavioral Design)
 - within always block
 - LHS must be reg

```
module some_circuit (  
    // inputs and outputs  
);  
    LHS      RHS  
    assign x = (a & b) | c;  
  
    always @(*)  
    begin  
        LHS      RHS  
        y = (a & b) | c;  
    end  
endmodule
```

Continuous

Procedural

Procedural Assignments

- Blocking assignment (=):
 - Executes sequentially, causing the next assignment to wait until the current assignment is completed.
- Nonblocking assignment (<=):
 - Executes concurrently, allowing multiple assignments to happen simultaneously without waiting for each other.

```
module some_circuit (  
    // inputs and outputs  
);  
  
always @(*)  
begin  
    Blocking Assignment  
    y = (a & b) | c;  
  
end  
endmodule
```


```
module some_circuit (  
    // inputs and outputs  
);  
  
always @(*)  
begin  
    Nonblocking Assignment  
    y <= (a & b) | c;  
  
end  
endmodule
```


Combinational logic + blocking



```
// Blocking assignments  
always @(a, b, c)  
begin  
    x = a;  
    x = x ^ b;  
    x = x | c;  
end
```

The order matters!

 


 


Combinational logic + nonblocking

```
// Nonblocking assignments  
always @(a, b, c)  
begin  
    x <= a;  
    x <= x ^ b;  
    x <= x | c;  
end
```

 non sense circuit
should not design like that




Sequential logic + blocking

 

```
// Blocking assignment  
always @(posedge clk)  
begin  
    Q1 = D;  
    Q2 = Q1;  
end
```

 ➡ You must change code order to make it working properly




Sequential logic + nonblocking



```
// Nonblocking assignment  
always @(posedge clk)  
begin  
    Q1 <= D;  
    Q2 <= Q1;  
end
```

 shift register with 2
cascade DFFs
the order doesn't matter



Assignment suggestions

- Blocking assignments for combinational logic
 - continuous assignment
 - within always `@(*)` blocks.
- Nonblocking assignments for sequential logic
 - within always `@(posedge clk)`
 - or always `@(negedge clk)` blocks
- Don't mix blocking and nonblocking together within same always block

Practice(2)

- Try to construct a T flipflop with a reset input.
 - There would be a reset input port apart from other inputs(clk, T), while it enable the output of T flipflop is 1'b0, while it disable the circuit works as T flipflop
 - Do the design and verify the function of your design.
 - Create the constraint file, do the synthetic and implementation, generate the bitstream file and program the device, then test on the EGO1 develop board.

Practices(3)


- Can this JK flip-flop work?
- Try to use it implement a T flip-flop, do the design, create constraint file, generate the bitstream file and program the device.
- Can the T flip-flop work? Explain the reason.

$$Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$$

```
module J_K_Flip_Flop(  
    input Clk, J, K,  
    output reg Q, Qn  
);  
    always @(posedge Clk)  
        if({J, K} == 2'b10) //set  
            begin  
                {Q, Qn} <= 2'b10;  
            end  
        else if ({J, K}==2'b01) //reset  
            begin  
                {Q, Qn} = 2'b01;  
            end  
        else if({J, K} == 2'b11) //reverse  
            begin  
                Q <= Qn;  
                Qn <= Q;  
            end  
    end  
endmodule
```

Tips:

 - Constraints: if you want to use IO pin as clock, you should use the CLOCK_DEDICATED_ROUTE FALSE constraint in the .xdc file to demote the Error message to a (Critical) WARNING. NOTES: This (Critical) WARNING HERE could be ignored.



```
set_property IOSTANDARD LVCMOS33 [get_ports clk]
set_property IOSTANDARD LVCMOS33 [get_ports D]
set_property IOSTANDARD LVCMOS33 [get_ports Q]
set_property IOSTANDARD LVCMOS33 [get_ports Qn]
set_property PACKAGE_PIN P5 [get_ports clk]
set_property PACKAGE_PIN R1 [get_ports D]
set_property PACKAGE_PIN J2 [get_ports Q]
set_property PACKAGE_PIN K2 [get_ports Qn]
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets {clk_IBUF}]
```